

CS1050 - Computer Organization and Digital Design

Lab 9 & 10 Nano Processor Design Competition

▪ **Group 20**

- Kariyapperuma K.M.N.S 230317J
 - Kirindage S.S 230336P
 - Jayasinghe J.D.D.S 230281P
 - Rafi M.A.A 230505J
-

♦ **Introduction**

- The objective of the lab task was to design a nano processor using the components we had previously studied in earlier lab sessions. It was a group project, with each team consisting of four members.
- We developed two different versions of the nano processor. Initially, we created a version that met only the basic requirements outlined in the lab manual. For this version, we incorporated components such as a 4-bit Add/Subtract unit, a 3-bit adder, a 3-bit Program Counter, 8-way 2-bit multiplexers, 2-way 3-bit multiplexers, 2-way 4-bit multiplexers, a Register Bank, a Program ROM, and an Instruction Decoder.
- For the extended version of the nano processor, we upgraded several key components to enhance functionality. The Register Bank, 8-way multiplexers, and Add/Subtract unit were expanded to 8 bits. We also integrated a multiplier unit to support more complex arithmetic operations. For better output representation, three 7-segment display units were used, with the ability to display negative values using a minus sign. Additionally, we designed a Program ROM capable of storing up to 16 instructions, allowing for more versatile and extended program execution.
- We used 2's complement representation for signed register values, while the basic version displays them as unsigned on the 7-segment display.

Table of Contents

Introduction.....	Page 1
-------------------	--------

1.Design with Minimum Qualifications

Executable Instruction.....	Page 4
-----------------------------	--------

Assembly Code & Machine Code for the Design	Page 4
---	--------

Design Components.....	Page 5
------------------------	--------

1. Nano Processor.....	Page 6
------------------------	--------

2. Program Counter.....	Page 12
-------------------------	---------

3. Program ROM.....	Page 15
---------------------	---------

4. MUX 2way 3bit.....	Page 18
-----------------------	---------

5. Instruction Decoder.....	Page 21
-----------------------------	---------

6. Register Bank.....	Page 25
-----------------------	---------

7. Decoder 3 to 8.....	Page 30
------------------------	---------

8. Decoder 2 to 4.....	Page 32
------------------------	---------

9. Register 4 bit.....	Page 33
------------------------	---------

10. MUX 2 way 4bit.....	Page 35
-------------------------	---------

11. MUX 8 way 4bit.....	Page 38
-------------------------	---------

12. Slow Clk.....	Page 41
-------------------	---------

13. Constraint File.....	Page 43
--------------------------	---------

Resource Utilization.....	Page 44
---------------------------	---------

2. Design with Extended Qualifications

Executable Instruction Set.....	Page 45
---------------------------------	---------

Design Components.....	Page 46
------------------------	---------

1. Improved Nano Processor.....	Page 47
---------------------------------	---------

2. Instruction Decoder.....	Page 54
-----------------------------	---------

3. Add/Sub 8-bit.....	Page 59
-----------------------	---------

4. Display 7-Segment.....	Page 63
---------------------------	---------

5. Multiplier 8bit.....	Page 66
6. Program_ROM.....	Page 70
7. LUT 16 7seg.....	Page 70
8. Constraint File.....	Page 72
Contributions.....	Page 73
Conclusion.....	Page 73

1) Design with Minimum qualifications

◆ Executable Instruction Set

Instruction	Description	Format (12-bit instruction)
MOVI R, <i>d</i>	Move immediate value <i>d</i> to register R, i.e., $R \leftarrow d$ $R \in [0, 7], d \in [0, 15]$	1 0 R R R 0 0 0 d d d d
ADD Ra, Rb	Add values in registers Ra and Rb and store the result in Ra, i.e., $Ra \leftarrow Ra + Rb$ $Ra, Rb \in [0, 7]$	0 0 Ra Ra Ra Rb Rb Rb 0 0 0 0
NEG R	2's complement of registers R, i.e., $R \leftarrow -R$ $R \in [0, 7]$	0 1 R R R 0 0 0 0 0 0 0
JZR R, d	Jump if value in register R is 0, i.e., If $R == 0$ $PC \leftarrow d$; Else $PC \leftarrow PC + 1$; $R \in [0, 7], d \in [0, 7]$	1 1 R R R 0 0 0 0 d d d

◆ Assembly Code & Machine Code for the Design

Process => $3 + 2 + 1 = 6$

"101110000001", -- 0	MOVI R7,1
"100010000010", -- 1	MOVI R1,2
"100100000011", -- 2	MOVI R2,3
"001110010000", -- 3	ADD R7,R1
"001110100000", -- 4	ADD R7,R2
"110000000111", -- 5	JZR R0,7
"110000000111", -- 6	JZR R0,7
"110000000111" -- 7	JZR R0,7

Design Components

 


Figure 1 – High-level diagram of the nanoprocessor.

1. Nano Processor

- Design Source VHDL Code of Nano Processor

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Nanoprocessor is
    Port ( Reset : in STD_LOGIC;
          Clock : in STD_LOGIC;
          R7_LED : out STD_LOGIC_VECTOR (3 downto 0);
          Zero_LED : out STD_LOGIC;
          Over_F_LED : out STD_LOGIC;
          Anode : out STD_LOGIC_VECTOR (3 downto 0);
          R7_7seg : out STD_LOGIC_VECTOR (6 downto 0));
end Nanoprocessor;

architecture Behavioral of Nanoprocessor is

    ----- Components -----

    ----- Slow Clock >>>> Slowed Clock signal so easy to observe -----
    component Slow_Clk is
        Port ( Clk_in : in STD_LOGIC;
              Clk_out : out STD_LOGIC);
    end component;

    -----Instruction Decoder-----
    component Instruction_Decoder is
        Port ( Instruction : in STD_LOGIC_VECTOR (11 downto 0);
              Jump_reg_val : in STD_LOGIC_VECTOR (3 downto 0); --register value for jump check
              Reg_Sel_A : out STD_LOGIC_VECTOR (2 downto 0); --Mux Select signal
              Reg_Sel_B : out STD_LOGIC_VECTOR (2 downto 0); --Muc Selct signal
              Reg_En : out STD_LOGIC_VECTOR (2 downto 0); --Register Bank write enable signal
              Flag_Reg_En : out STD_LOGIC; -- Enable for ADD_SUB_Units Flag
              Jump_Address : out STD_LOGIC_VECTOR (2 downto 0);
              Jump_Flag : out STD_LOGIC;
              Add_Sub_Sel : out STD_LOGIC; -- 0 for add , 1 for subtract
              Load_Sel : out STD_LOGIC; -- 0 for immediarte value, 1 for add_sub unit value
              Immediate_Value : out STD_LOGIC_VECTOR (3 downto 0));
    end component;

    ----- Register Bank (8 4-bit registers) -----
    component Reg_Bank is
        Port ( RegSel : in STD_LOGIC_VECTOR (2 downto 0); --Register Select signal
              D : in STD_LOGIC_VECTOR (3 downto 0); --Data line
              Reset : in STD_LOGIC;
              Clk : in STD_LOGIC;
              R0 : out STD_LOGIC_VECTOR (3 downto 0);
              R1 : out STD_LOGIC_VECTOR (3 downto 0);
              R2 : out STD_LOGIC_VECTOR (3 downto 0);
              R3 : out STD_LOGIC_VECTOR (3 downto 0);
              R4 : out STD_LOGIC_VECTOR (3 downto 0);
              R5 : out STD_LOGIC_VECTOR (3 downto 0);
              R6 : out STD_LOGIC_VECTOR (3 downto 0);
              R7 : out STD_LOGIC_VECTOR (3 downto 0));
    end component;

    ----- Flag Register (Zero, Overflow) -----
    component Flag_register is
        Port ( Zero : in STD_LOGIC; --zero signal from ADD_SUB_Unit
              Over_f : in STD_LOGIC; --overflow signal from ADD_SUB_Unit
              En : in STD_LOGIC;
              reset : in STD_LOGIC;
              Clk : in STD_LOGIC;
```

```

        Zero_Flag : out STD_LOGIC;
        OverFlow_Flag : out STD_LOGIC);
end component;

---- Program Counter (register) -----
component Program_Counter is
    Port ( D : in STD_LOGIC_VECTOR (2 downto 0);
          Reset : in STD_LOGIC;
          Clk : in STD_LOGIC;
          P_count : out STD_LOGIC_VECTOR (2 downto 0));
end component;

---- 4-bit ADD_SUB_Unit -----
component ADD_SUB_4bit is
    Port ( Ins : in STD_LOGIC; -- instruction (ADD =0, SUB = 1) (also works as C_in)
          A : in STD_LOGIC_VECTOR (3 DOWNTO 0);
          B : in STD_LOGIC_VECTOR (3 DOWNTO 0);
          S : out STD_LOGIC_VECTOR (3 DOWNTO 0);
          O_flow : out STD_LOGIC;
          Zero: out STD_LOGIC);
end component;

---- 3-bit Adder -----
component Adder_3bit is
    Port (
          A : in STD_LOGIC_VECTOR (2 DOWNTO 0);
          B : in STD_LOGIC_VECTOR (2 DOWNTO 0);
          S : out STD_LOGIC_VECTOR (2 DOWNTO 0));
end component;

---- 8 way 4bit Multiplexer -----
component Mux_8way_4bit is
    Port ( S : in STD_LOGIC_VECTOR (2 downto 0);
          L0 : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit Input Line 0
          L1 : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit Input Line 1
          L2 : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit Input Line 2
          L3 : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit Input Line 3
          L4 : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit Input Line 4
          L5 : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit Input Line 5
          L6 : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit Input Line 6
          L7 : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit Input Line 7
          EN : in STD_LOGIC;
          OL: out STD_LOGIC_VECTOR (3 downto 0)); -- 4-bit output line
end component;

---- 2 way 4bit Multiplexer -----
component Mux_2way_4bit is
    Port (
          Sel : in STD_LOGIC;
          A : in STD_LOGIC_VECTOR (3 downto 0);
          B : in STD_LOGIC_VECTOR (3 downto 0);
          Mux_out : out STD_LOGIC_VECTOR (3 downto 0));
end component;

---- 2 way 3bit Multiplexer -----
component Mux_2way_3bit is
    Port (
          Sel : in STD_LOGIC;
          A : in STD_LOGIC_VECTOR (2 downto 0);
          B : in STD_LOGIC_VECTOR (2 downto 0);
          Mux_out : out STD_LOGIC_VECTOR (2 downto 0));
end component;

----- Program ROM >>>> Stored Machine language Assembly code -----
component Program_ROM is
    Port ( address : in STD_LOGIC_VECTOR (2 downto 0);
          data : out STD_LOGIC_VECTOR (11 downto 0));
end component;

---- Lookup table for 7 Segment display outputs ----
component LUT_16_7seg is
    Port ( address : in STD_LOGIC_VECTOR (3 downto 0);
          data : out STD_LOGIC_VECTOR (6 downto 0));

```

```

end component;

-----Signals-----

signal Slow_clock :std_logic;
signal instruction : std_logic_vector (11 downto 0);
signal Mux_A_out ,Mux_B_out : std_logic_vector (3 downto 0); -- 8way MUX outputs
signal Mux_A_Sel, Mux_B_Sel : std_logic_vector (2 downto 0); -- 8way MUX Select signal
signal Reg_EN : std_logic_vector (2 downto 0); -- Register bank select reg for write enable signal
signal Flag_Reg_EN : std_logic; --flag register enable signal
signal Address_to_jump : std_logic_vector (2 downto 0);
signal Jump_Flag : std_logic;
signal Add_Sub_Sel : std_logic;
signal Load_Sel : std_logic; -- load select for register write data bus
signal Immediate_Value: std_logic_vector (3 downto 0);

signal Reg_Data_in: std_logic_vector (3 downto 0); --Register Data in Bus
--Register Data outs
signal Reg_0, Reg_1, Reg_2, Reg_3, Reg_4, Reg_5, Reg_6, Reg_7: std_logic_vector (3 downto 0);
signal Add_Sub_Out : std_logic_vector (3 downto 0);
signal O_flow, Zero : std_logic;

signal Program_C_in, Program_C_out: std_logic_vector (2 downto 0);
signal Program_C_Incrementer_out : std_logic_vector (2 downto 0);

begin

    SlowClock : Slow_Clk
    port map(
        Clk_in => Clock,
        Clk_out => Slow_clock );

    Instruction_Decoder_0: Instruction_Decoder
    port map(
        Instruction      => instruction,
        Jump_reg_val     => Mux_A_out,
        Reg_Sel_A        => Mux_A_Sel,
        Reg_Sel_B        => Mux_B_Sel,
        Reg_En           => Reg_EN,
        Flag_Reg_En      => Flag_Reg_EN,
        Jump_Address     => Address_to_jump,
        Jump_Flag        => Jump_Flag,
        Add_Sub_Sel      => Add_Sub_Sel,
        Load_Sel         => Load_Sel,
        Immediate_Value => Immediate_Value);

    Register_Bank_0 : Reg_Bank
    port map(
        RegSel  => Reg_EN,
        D       => Reg_Data_in,
        Reset   => Reset,
        Clk     => Slow_clock,
        R0      => Reg_0,
        R1      => Reg_1,
        R2      => Reg_2,
        R3      => Reg_3,
        R4      => Reg_4,
        R5      => Reg_5,
        R6      => Reg_6,
        R7      => Reg_7);

    Mux_8way_4bit_A: Mux_8way_4bit
    port map(
        S => Mux_A_Sel,
        L0 => Reg_0,
        L1 => Reg_1,
        L2 => Reg_2,
        L3 => Reg_3,
        L4 => Reg_4,
        L5 => Reg_5,

```



```

L6 => Reg_6,
L7 => Reg_7,
EN => '1',
OL => Mux_A_out);

Mux_8way_4bit_B: Mux_8way_4bit
port map(
  S => Mux_B_Sel,
  L0 => Reg_0,
  L1 => Reg_1,
  L2 => Reg_2,
  L3 => Reg_3,
  L4 => Reg_4,
  L5 => Reg_5,
  L6 => Reg_6,
  L7 => Reg_7,
  EN => '1',
  OL => Mux_B_out);

ADD_SUB_UNIT: Add_Sub_4bit
port map(
  Ins => Add_Sub_Sel,
  A   => Mux_A_out,
  B   => Mux_B_out,
  S   => Add_Sub_Out,
  O_flow => O_flow,
  Zero  => Zero);

Mux_for_Reg_Write_Data_Bus: Mux_2way_4bit
port map(
  A => Immediate_Value,
  B => Add_Sub_Out,
  Sel => Load_Sel,
  Mux_out => Reg_Data_in);

Flag_Register_0 :Flag_register
port map(
  Zero  => Zero,
  Over_f => O_flow,
  En    => Flag_Reg_EN,
  reset => Reset,
  Clk   => Slow_clock,
  Zero_Flag => Zero_LED,
  Overflow_Flag => Over_F_LED);

Program_Counter_0: Program_Counter
port map(
  D      => Program_C_in,
  Reset  => Reset,
  Clk    => Slow_clock,
  P_count => Program_C_out);

Program_Count_Incrementer: Adder_3bit
port map(
  A => Program_C_out,
  B => "001",
  S => Program_C_Incrementer_out);

Mux_2way_3bit_0 : Mux_2way_3bit
port map(
  A => Program_C_Incrementer_out,
  B => Address_to_jump,
  Sel => Jump_Flag,
  Mux_out => Program_C_in);

Program_ROM_0: Program_ROM
Port map(
  address => Program_C_out,
  data    => instruction);

---- Output Settings -----

-- Zero and Overflow outputs done in above

```

```

LUT_16_7seg_0 : LUT_16_7seg
  Port map(
    address => Reg_7,
    data    => R7_7seg);


R7_LED  <= Reg_7;

----enable left most 7 segment display panel---
anode <= "1110";

end Behavioral;

```

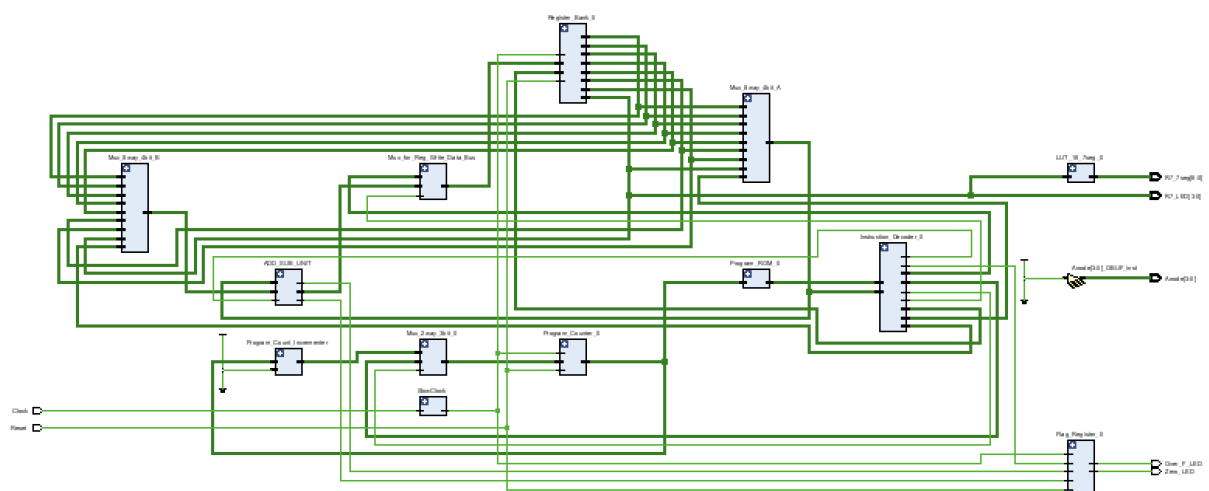● RTL Schematic Diagram of the Nano Processor



● Behavioral Simulation Code for Nano Processor

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_Nanoprocessor is
end TB_Nanoprocessor;

architecture Behavioral of TB_Nanoprocessor is

  component Nanoprocessor is
    Port (
      Reset : in STD_LOGIC;
      Clock : in STD_LOGIC;
      R7_LED : out STD_LOGIC_VECTOR (3 downto 0);
      Zero_LED : out STD_LOGIC;
      Over_F_LED : out STD_LOGIC;
      Anode : out STD_LOGIC_VECTOR (3 downto 0);
      R7_7seg : out STD_LOGIC_VECTOR (6 downto 0));
  end component;

  signal reset : std_logic;
  signal clk : std_logic := '0';
  signal Zero_LED, Over_F_LED : std_logic;
  signal R7_LED : STD_LOGIC_VECTOR (3 downto 0);
  signal anode : STD_LOGIC_VECTOR (3 downto 0);
  signal R7_7seg : STD_LOGIC_VECTOR (6 downto 0);

end Behavioral;

```

```

begin

UUT: Nanoprocessor
  port map(
    Reset    => reset,
    Clock    => clk,
    R7_LED   => R7_LED,
    Zero_LED  => Zero_LED,
    Over_F_LED => Over_F_LED,
    Anode    => anode,
    R7_7seg  => R7_7seg);

  process
  begin
    clk <= not clk;
    wait for 5 ns;
  end process;

  process
  begin
    reset <= '1';
    wait for 100ns;

    reset <= '0';
    wait;
  end process;

end Behavioral;

```

● Timing Diagram for Nano Processor



2. Program Counter

- Design Source VHDL Code of Program Counter

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Program_Counter is
    Port ( D : in STD_LOGIC_VECTOR (2 downto 0);
          Reset : in STD_LOGIC;
          Clk : in STD_LOGIC;
          P_count : out STD_LOGIC_VECTOR (2 downto 0));
end Program_Counter;


architecture Behavioral of Program_Counter is

begin

process (Clk) begin
    if (rising_edge(Clk)) then
        if Reset = '1' then
            P_count <= "000";
        else
            P_count <= D;
        end if;
    end if;
end process;

end Behavioral;
```

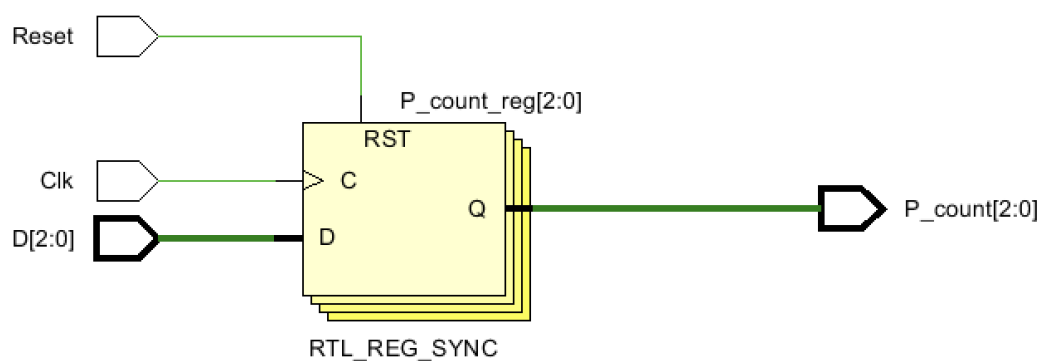- RTL Schematic Diagram of the Program Counter



Behavioral Simulation Code for Program Counter

```
entity TB_Program_Counter is
-- Port ( );
end TB_Program_Counter;

architecture Behavioral of TB_Program_Counter is

component Program_Counter is
    Port (
        D : in STD_LOGIC_VECTOR (2 downto 0);
        Reset : in STD_LOGIC;
        Clk : in STD_LOGIC;
        P_count : out STD_LOGIC_VECTOR (2 downto 0));
end component;

signal D, P_count : STD_LOGIC_VECTOR (2 downto 0);
signal Reset, Clk: STD_LOGIC;

component Slow_Clk
    Port ( Clk_in : in STD_LOGIC;
           Clk_out : out STD_LOGIC);
end component;

signal Clk_in : STD_LOGIC:= '0' ;
signal Clk_out : STD_LOGIC;

begin

UUT: Program_Counter
    port map (
        D=>D,
        Reset=>Reset,
        Clk=>Clk,
        P_count=>P_count
    );

-- Instantiate the Unit Under Test (UUT)
Clock_UUT: Slow_Clk
    Port map (
        Clk_in => Clk_in,
        Clk_out => Clk_out
    );

-- Generate 5 rising edges (5 clock cycles)
Clock_process: process
begin
    Clk_in <= not Clk_in;
    wait for 5 ns; -- 10ns full period = 100 MHz
end process;
Clk <= Clk_out;
process
begin

-- Test case 1: SEL = 0, Y should be A
    D <= "011";
    Reset<= '0';
    wait for 200 ns;

-- Test case 2: SEL = 1, Y should be B
    D <= "101";
    wait for 200 ns;
```

```
        D <= "110";
        wait for 200 ns;
        Reset<= '1';
        wait for 200 ns;
        Reset<= '0';
        D <= "010";
        wait for 200 ns;
        D <= "100";

    wait;
    end process;

end Behavioral;
```

3. Program ROM

- Design Source VHDL Code of Program ROM

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- arithmetic functions with Signed or Unsigned values
use IEEE.NUMERIC_STD.ALL;

entity Program_ROM is
    Port ( address : in STD_LOGIC_VECTOR (2 downto 0);
          data : out STD_LOGIC_VECTOR (11 downto 0));
end Program_ROM;

architecture Behavioral of Program_ROM is


    type rom_type is array (0 to 7) of std_logic_vector(11 downto 0);

    signal Program_ROM : rom_type := (
        "101110000001", -- 0      MOVI R7,1
        "100010000010", -- 1      MOVI R1,2
        "100100000011", -- 2      MOVI R2,3
        "001110010000", -- 3      ADD R7,R1
        "001110100000", -- 4      ADD R7,R2
        "110000000111", -- 5      JZR R0,7
        "110000000111", -- 6      JZR R0,7
        "110000000111" -- 7      JZR R0,7
    );

begin
    data <= Program_ROM(to_integer(unsigned(address)));

end Behavioral;
```

 - RTL Schematic Diagram of the Program ROM



- Behavioral Simulation Code for Program ROM

```
entity TB_Program_ROM is
Port ( );
end TB_Program_ROM;

architecture Behavioral of TB_Program_ROM is

    component Program_ROM is
        Port ( address : in STD_LOGIC_VECTOR (2 downto 0);
              data : out STD_LOGIC_VECTOR (11 downto 0));
    end component;

    signal address : STD_LOGIC_VECTOR (2 downto 0);
    signal data : STD_LOGIC_VECTOR (11 downto 0);

begin

    UUT: Program_ROM
    port map (
        address=>address,
        data=> data
    );

    process
    begin

        address <= "000";
        wait for 200 ns;


        address <= "001";
        wait for 200 ns;
        address <= "010";

        wait for 200 ns;
        address <= "011";

        wait;
    end process;

end Behavioral;
```


- Timing Diagram for MUX_Program ROM

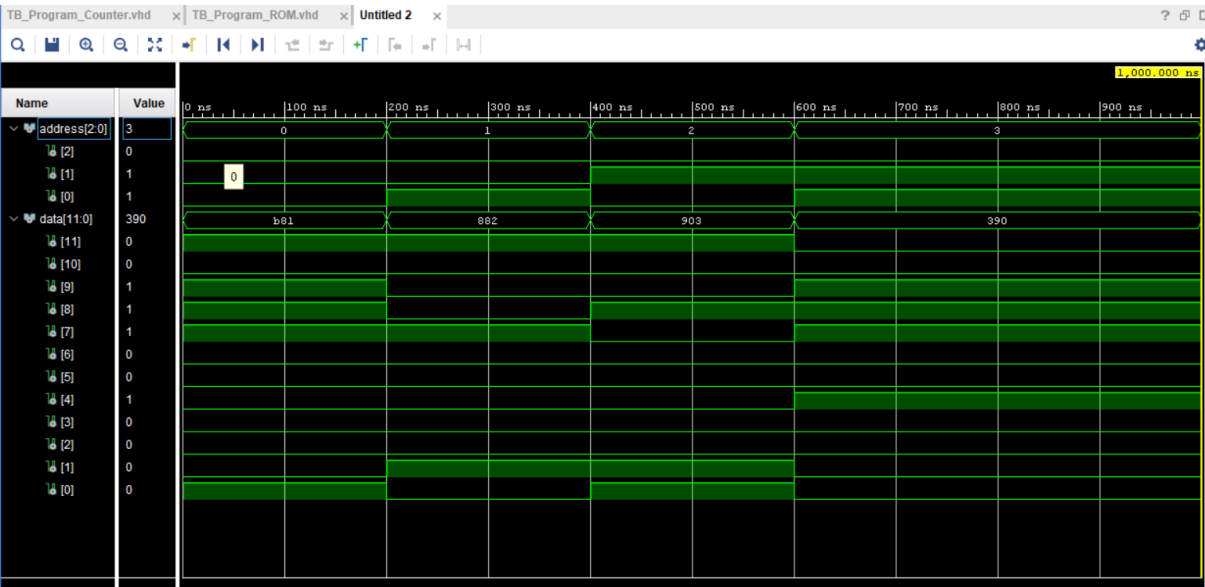

4. MUX_2way_3bit

- Design Source VHDL Code of MUX_2way_3bit

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity Mux_2way_3bit is
    Port ( Sel : in STD_LOGIC;
          A : in STD_LOGIC_VECTOR (2 downto 0);
          B : in STD_LOGIC_VECTOR (2 downto 0);
          Mux_out : out STD_LOGIC_VECTOR (2 downto 0));
end Mux_2way_3bit;


architecture Behavioral of Mux_2way_3bit is

begin
    --Sel=0 for A, Sel=1 for B

    Mux_out(0) <= (A(0) AND (NOT Sel)) or (B(0) AND Sel);
    Mux_out(1) <= (A(1) AND (NOT Sel)) or (B(1) AND Sel);
    Mux_out(2) <= (A(2) AND (NOT Sel)) or (B(2) AND Sel);

end Behavioral;
```

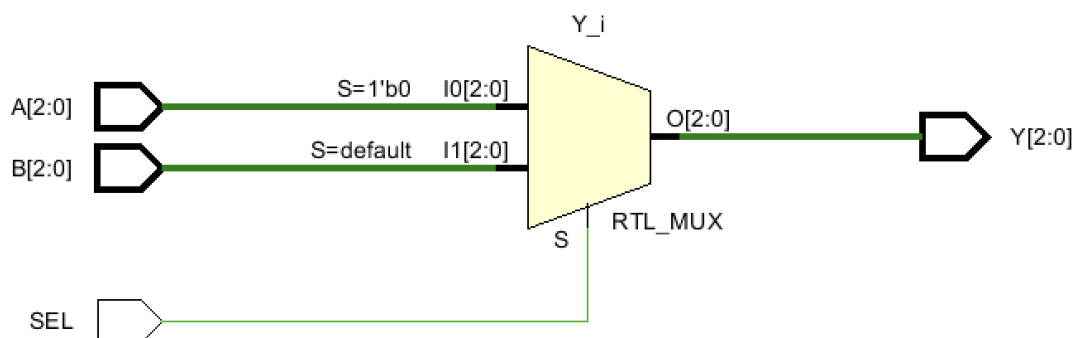- RTL Schematic Diagram of the MUX_2way_3bit



- Behavioral Simulation Code for MUX_2way_3bit

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_Mux_2way_3bit is
end TB_Mux_2way_3bit;

architecture Behavioral of TB_Mux_2way_3bit is

    -- Component declaration
    component Mux_2way_3bit is
        Port (
            A : in  STD_LOGIC_VECTOR(2 downto 0);
            B : in  STD_LOGIC_VECTOR(2 downto 0);
            SEL : in  STD_LOGIC;
            Y : out STD_LOGIC_VECTOR(2 downto 0)
        );
    end component;

    -- Testbench signals
    signal A_tb, B_tb, Y_tb : STD_LOGIC_VECTOR(2 downto 0);
    signal SEL_tb : STD_LOGIC;

begin

    -- Instantiate the Unit Under Test (UUT)
    UUT: Mux_2way_3bit
        port map (
            A => A_tb,
            B => B_tb,
            SEL => SEL_tb,
            Y => Y_tb
        );

    -- Stimulus process
    process
    begin
        -- Test case 1: SEL = 0, Y should be A
        A_tb <= "101";
        B_tb <= "011";
        SEL_tb <= '0';
        wait for 100 ns;

        -- Test case 2: SEL = 1, Y should be B
        SEL_tb <= '1';
        wait for 100 ns;


        -- Test case 3: Change inputs
        A_tb <= "001";
        B_tb <= "111";
        SEL_tb <= '0';
        wait for 100 ns;

        SEL_tb <= '1';
        wait for 100 ns;

        -- Finish
        wait;
    end process;

end Behavioral;
```

● Timing Diagram for MUX_2way_3bit

 

5. Instruction Decoder

- Design Source VHDL Code of Instruction Decoder

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Instruction_Decoder is
    Port ( Instruction : in STD_LOGIC_VECTOR (11 downto 0);
          Jump_reg_val : in STD_LOGIC_VECTOR (3 downto 0); --register value for jump check
          Reg_Sel_A: out STD_LOGIC_VECTOR (2 downto 0); --Mux Select signal
          Reg_Sel_B: out STD_LOGIC_VECTOR (2 downto 0); --Mux Select signal
          Reg_En :out STD_LOGIC_VECTOR (2 downto 0); --Register Bank write enable signal
          Flag_Reg_En : out STD_LOGIC; -- Enable for ADD_SUB_Units Flag
          Jump_Address : out STD_LOGIC_VECTOR (2 downto 0);
          Jump_Flag : out STD_LOGIC;
          Add_Sub_Sel : out STD_LOGIC; -- 0 for add , 1 for subtract
          Load_Sel : out STD_LOGIC; -- 0 for immediate value, 1 for add_sub unit value
          Immediate_Value : out STD_LOGIC_VECTOR (3 downto 0));
end Instruction_Decoder;

architecture Behavioral of Instruction_Decoder is

    --signal Op_code : STD_LOGIC_VECTOR (1 downto 0);

begin

    Process (Instruction, Jump_reg_val)
    begin


        if Instruction (11 downto 10) = "00" then -- ADD
            Jump_Flag <= '0';
            Reg_Sel_A <= Instruction(9 downto 7);
            Reg_Sel_B <= Instruction(6 downto 4);
            Add_Sub_Sel <= '0';
            Load_Sel <= '1';
            Reg_En <= Instruction(9 downto 7);
            Flag_Reg_En <= '1';

        elsif Instruction (11 downto 10) = "01" then -- Neg
            Jump_Flag <= '0';
            Reg_Sel_A <= Instruction(9 downto 7);
            Reg_Sel_B <= Instruction(6 downto 4);
            Add_Sub_Sel <= '1';
            Load_Sel <= '1';
            Reg_En <= Instruction(9 downto 7);
            Flag_Reg_En <= '1';

        elsif Instruction (11 downto 10) = "10" then -- MOVI
            Jump_Flag <= '0';
            Load_Sel <= '0';
            Reg_En <= Instruction(9 downto 7);
            Flag_Reg_En <= '0';
            Immediate_value <= Instruction(3 downto 0);

        elsif Instruction (11 downto 10) = "11" then --JZR
            Reg_En <= "000";
            Flag_Reg_En <= '0';
            Reg_Sel_A <= Instruction(9 downto 7);
            if Jump_reg_val = "0000" then
                Jump_Flag <= '1';
                Jump_Address <= Instruction (2 downto 0);
            else
                Jump_Flag <= '0';
            end if;
        end if;
    end process;
end Behavioral;
```

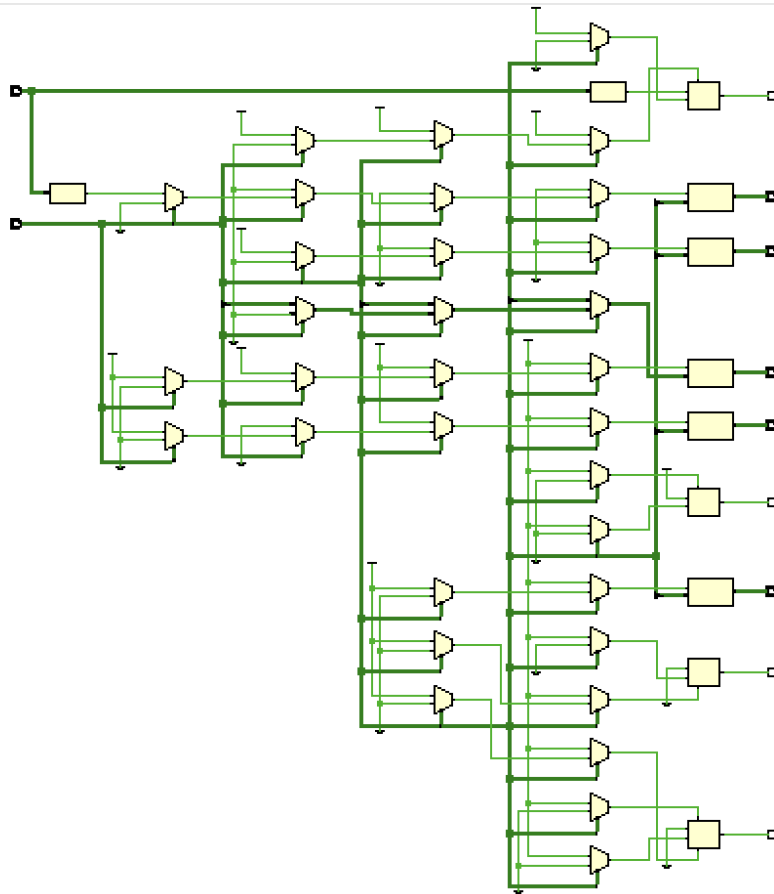- RTL Schematic Diagram of the Instruction Decoder



- Behavioral Simulation Code for Instruction Decoder

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity TB_Instruction_Decorder is
-- Port ( );
end TB_Instruction_Decorder;

architecture Behavioral of TB_Instruction_Decorder is

component Instruction_Decoder is
Port ( Instruction : in STD_LOGIC_VECTOR (11 downto 0);
      Jump_reg_val : in STD_LOGIC_VECTOR (3 downto 0); --register value for jump check
      Reg_Sel_A: out STD_LOGIC_VECTOR (2 downto 0);    --Mux Select signal
      Reg_Sel_B: out STD_LOGIC_VECTOR (2 downto 0);    --Muc Selct signal
      Reg_En :out STD_LOGIC_VECTOR (2 downto 0);      --Register Bank write enable signal
      Flag_Reg_En : out STD_LOGIC;                    -- Enable for ADD_SUB_Units Flag
      Jump_Address : out STD_LOGIC_VECTOR (2 downto 0);
      Jump_Flag : out STD_LOGIC;
      Add_Sub_Sel : out STD_LOGIC; -- 0 for add , 1 for subtract
      Load_Sel : out STD_LOGIC;    -- 0 for immediarte value, 1 for add_sub unit value
      Immediate_Value : out STD_LOGIC_VECTOR (3 downto 0));
end component;

signal Instruction : STD_LOGIC_VECTOR (11 downto 0);
signal Jump_reg_val ,Immediate_Value: STD_LOGIC_VECTOR (3 downto 0);
```

```

signal Reg_Sel_A, Reg_Sel_B, Reg_En , Jump_Address : STD_LOGIC_VECTOR (2 downto 0);
signal Flag_Reg_En, Load_Sel, Add_Sub_Sel, Jump_Flag : STD_LOGIC;

begin

UUT:Instruction_Decoder
    port map (
        Instruction=>Instruction,
        Jump_reg_val=>Jump_reg_val,
        Reg_Sel_A=> Reg_Sel_A,
        Reg_Sel_B=> Reg_Sel_B,
        Reg_En=> Reg_En,
        Flag_Reg_En=>Flag_Reg_En,
        Jump_Address=>Jump_Address,
        Jump_Flag=>Jump_Flag,
        Add_Sub_Sel=>Add_Sub_Sel,
        Load_Sel =>Load_Sel ,
        Immediate_Value=>Immediate_Value );

    process
    begin

        Jump_reg_val <= "0000";
        Instruction <="101110000011"; -- MOVI R7,1
        wait for 100ns;

        Instruction <="100010000010"; -- MOVI R1,2
        wait for 100ns;

        Instruction <= "100100000011"; --MOVI R2,3
        wait for 100ns;

        Instruction <="110010000111"; -- JZR R0,7
        wait for 100ns;

        Instruction <="001110010000"; -- ADD R7,R1
        wait for 100ns;

        Instruction <="010010000000"; -- NEG R1
        wait for 100ns;

        Jump_reg_val <= "0100";
        Instruction <="110100000101"; -- JZR R2,5


        wait;

    end process;

end Behavioral;

```

● Timing Diagram for Instruction Decoder

 

6. Register Bank

- Design Source VHDL Code of Register Bank

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity Reg_Bank is
  Port ( RegSel : in STD_LOGIC_VECTOR (2 downto 0);  --Register Select signal
        D : in STD_LOGIC_VECTOR (3 downto 0);      --Data line
        Reset: in STD_LOGIC;
        Clk : in STD_LOGIC;
        R0 : out STD_LOGIC_VECTOR (3 downto 0);
        R1 : out STD_LOGIC_VECTOR (3 downto 0);
        R2 : out STD_LOGIC_VECTOR (3 downto 0);
        R3 : out STD_LOGIC_VECTOR (3 downto 0);
        R4 : out STD_LOGIC_VECTOR (3 downto 0);
        R5 : out STD_LOGIC_VECTOR (3 downto 0);
        R6 : out STD_LOGIC_VECTOR (3 downto 0);
        R7 : out STD_LOGIC_VECTOR (3 downto 0));
end Reg_Bank;

architecture Behavioral of Reg_Bank is

  component Reg is
    Port ( D : in STD_LOGIC_VECTOR (3 downto 0);
          En : in STD_LOGIC;
          Res : in STD_LOGIC;
          Clk : in STD_LOGIC;
          Q : out STD_LOGIC_VECTOR (3 downto 0));
  end component;

  component Decoder_3_to_8 is
    Port ( I : in STD_LOGIC_VECTOR (2 downto 0);
          EN : in STD_LOGIC;
          Y : out STD_LOGIC_VECTOR (7 downto 0));
  end component;

  signal line_en : STD_LOGIC_VECTOR (7 downto 0);

begin

  Decode: Decoder_3_to_8
    port map(
      I => RegSel,
      En => '1',
      Y => line_en);

  R0 <= "0000";  --hard code R0 to 0000

  Reg1: Reg
    port map(
      D => D,
      En => line_en(1),
      Res => Reset,
      Clk => Clk,
      Q => R1);

  Reg2: Reg
    port map(
      D => D,
      En => line_en(2),
```

```

        Res => Reset,
        Clk => Clk,
        Q => R2);

Reg3: Reg
    port map(
        D => D,
        En => line_en(3),
        Res => Reset,
        Clk => Clk,
        Q => R3);

Reg4: Reg
    port map(
        D => D,
        En => line_en(4),
        Res => Reset,
        Clk => Clk,
        Q => R4);

Reg5: Reg
    port map(
        D => D,
        En => line_en(5),
        Res => Reset,
        Clk => Clk,
        Q => R5);


Reg6: Reg
    port map(
        D => D,
        En => line_en(6),
        Res => Reset,
        Clk => Clk,
        Q => R6);

Reg7: Reg
    port map(
        D => D,
        En => line_en(7),
        Res => Reset,
        Clk => Clk,
        Q => R7);

end Behavioral;

```

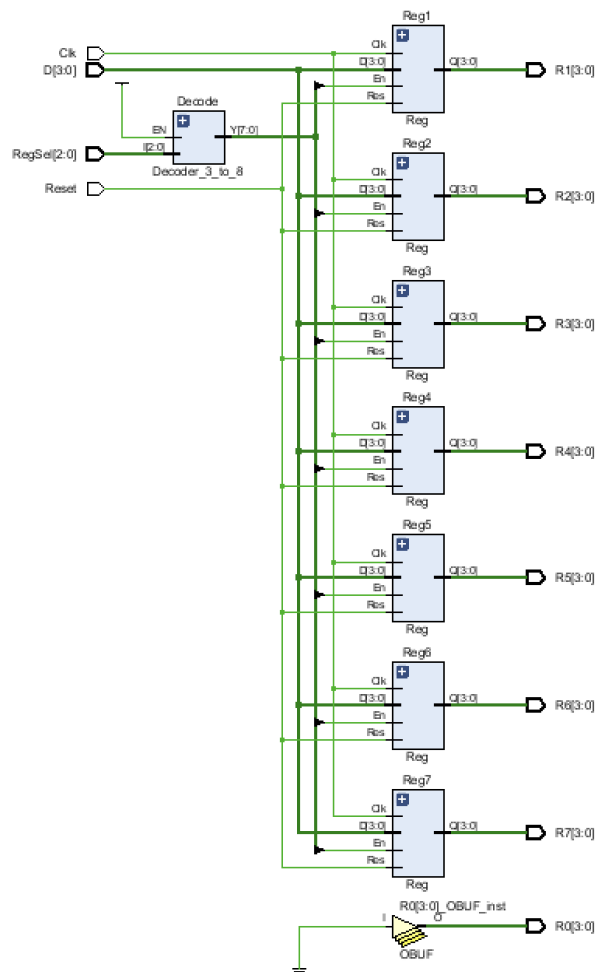- RTL Schematic Diagram of the Register Bank



- Behavioral Simulation Code for Register Bank

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_Register_Bank is
end TB_Register_Bank;

architecture Behavioral of TB_Register_Bank is
    component Reg_Bank is
        Port ( RegSel : in STD_LOGIC_VECTOR (2 downto 0); --Register Select signal
              D : in STD_LOGIC_VECTOR (3 downto 0); --Data line
              Reset: in STD_LOGIC;
              Clk : in STD_LOGIC;
              R0 : out STD_LOGIC_VECTOR (3 downto 0);
              R1 : out STD_LOGIC_VECTOR (3 downto 0);
              R2 : out STD_LOGIC_VECTOR (3 downto 0);
              R3 : out STD_LOGIC_VECTOR (3 downto 0);
              R4 : out STD_LOGIC_VECTOR (3 downto 0);
              R5 : out STD_LOGIC_VECTOR (3 downto 0);
              R6 : out STD_LOGIC_VECTOR (3 downto 0);
              R7 : out STD_LOGIC_VECTOR (3 downto 0));
    end component;

    -- Register Bank Component Instantiation
    Reg_Bank : component Reg_Bank
        port map (
            RegSel => RegSel,
            D => D,
            Reset => Reset,
            Clk => Clk,
            R0 => R0,
            R1 => R1,
            R2 => R2,
            R3 => R3,
            R4 => R4,
            R5 => R5,
            R6 => R6,
            R7 => R7
        );
end architecture;
```

```

end component;

signal RegSel:STD_LOGIC_VECTOR (2 downto 0);
signal Reset,Clk: STD_LOGIC;
signal R0,D,R1,R2,R3,R4,R5,R6,R7 :STD_LOGIC_VECTOR (3 downto 0);

component Slow_Clk
  Port ( Clk_in : in STD_LOGIC;
         Clk_out : out STD_LOGIC);
end component;

signal Clk_in : STD_LOGIC:= '0' ;
signal Clk_out : STD_LOGIC;

begin

UUT: Reg_Bank
port map (
RegSel=>RegSel,
D=>D,
Reset=>Reset,
Clk=>Clk,
R0=>R0,
R1=>R1,
R2=>R2,
R3=>R3,
R4=>R4,
R5=>R5,
R6=>R6,
R7=>R7
);

-- Instantiate the Unit Under Test (UUT)
Clock_UUT: Slow_Clk
  Port map (
    Clk_in => Clk_in,
    Clk_out => Clk_out

  );

-- Generate 5 rising edges (5 clock cycles)
Clock_process: process
begin
  Clk_in <= not Clk_in;
  wait for 5 ns; -- 10ns full period = 100 MHz
end process;
Clk <= Clk_out;
process
begin
  RegSel<="001";
  Reset<='0';
  D<="1101";
  wait for 100 ns;

  RegSel<="010";
  D<="1001";
  wait for 100 ns;

```

```
        RegSel<="110";
        D<="1011";
        wait for 100 ns;
        Reset<='1';
    wait for 100 ns;
    Reset<='0';
    RegSel<="011";
    D<="0001";
    wait for 100 ns;

    RegSel<="111";
    D<="0011";
wait;
    end process;

end Behavioral;
```

7. Decoder_3_to_8

- Design Source VHDL Code of Decoder_3_to_8

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Decoder_3_to_8 is
    Port ( I : in STD_LOGIC_VECTOR (2 downto 0);
          EN : in STD_LOGIC;
          Y : out STD_LOGIC_VECTOR (7 downto 0));
end Decoder_3_to_8;

architecture Behavioral of Decoder_3_to_8 is

    component Decoder_2_to_4
        Port ( I : in STD_LOGIC_VECTOR;
              EN : in STD_LOGIC;
              Y : out STD_LOGIC_VECTOR );
    end component;

    signal I0,I1 :std_logic_vector(1 downto 0);
    signal Y0, Y1 :std_logic_vector(3 downto 0);
    signal en0,en1 :std_logic;

begin


    Decoder_2_to_4_0:Decoder_2_to_4
    port map(
        I=>I0,
        EN=>en0,
        Y=>Y0);

    Decoder_2_to_4_1:Decoder_2_to_4
    port map(
        I=>I1,
        EN=>en1,
        Y=>Y1);

    en0<= NOT(I(2)) AND EN;
    en1<= I(2) AND EN;
    I0<= I(1 downto 0);
    I1<= I(1 downto 0);
    --I2<=I(2);
    Y(3 downto 0) <= Y0;
    Y(7 downto 4) <= Y1;

end Behavioral;
```

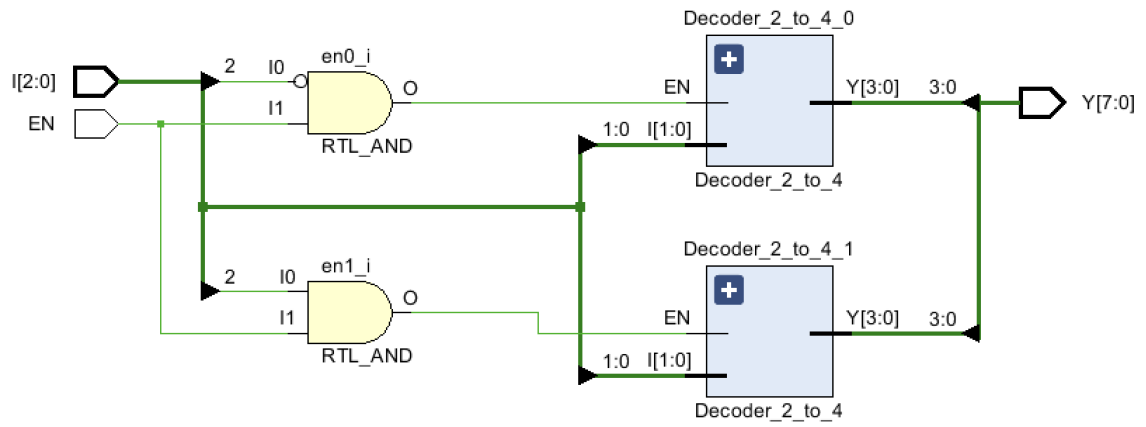- RTL Schematic Diagram of the Decoder_3_to_8



8. Decoder_2_to_4

- Design Source VHDL Code of Decoder_2_to_4

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Decoder_2_to_4 is
    Port ( I : in STD_LOGIC_VECTOR (1 downto 0);
          EN : in STD_LOGIC;
          Y : out STD_LOGIC_VECTOR (3 downto 0));
end Decoder_2_to_4;

architecture Behavioral of Decoder_2_to_4 is


    signal not_I0, not_I1 :std_logic;

begin
    not_I0 <= NOT I(0);
    not_I1 <= NOT I(1);

    Y(0) <= not_I0 AND not_I1 AND EN;
    Y(1) <= I(0) AND not_I1 AND EN;
    Y(2) <= not_I0 AND I(1) AND EN;
    Y(3) <= I(0) AND I(1) AND EN;

end Behavioral;
```

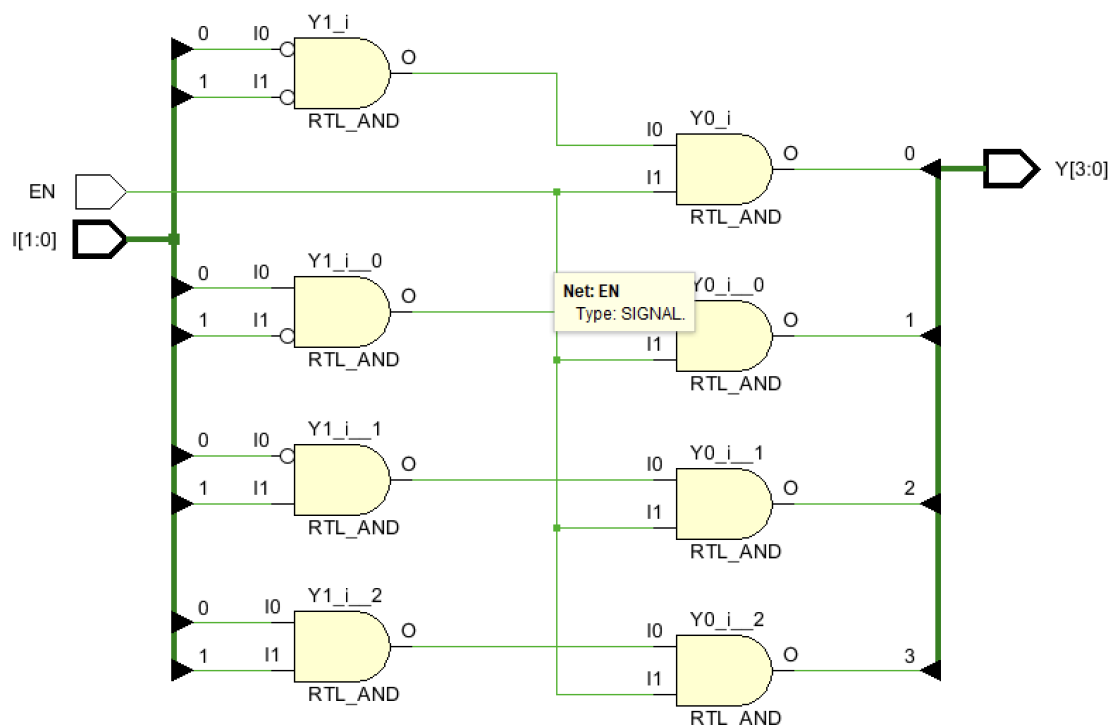- RTL Schematic Diagram of the Decoder_2_to_4



9. Register 4 bit

- Design Source VHDL Code of Register 4 bit

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity Reg is
  Port ( D : in STD_LOGIC_VECTOR (3 downto 0);
        En : in STD_LOGIC;
        Res : in STD_LOGIC;
        Clk : in STD_LOGIC;
        Q : out STD_LOGIC_VECTOR (3 downto 0));
end Reg;


architecture Behavioral of Reg is

begin

process (Clk) begin
  if (rising_edge(Clk)) then
    if Res = '1' then
      Q <= "0000";
    elsif En = '1' then
      Q <= D;
    end if;
  end if;
end process;

end Behavioral;
```

 - RTL Schematic Diagram of the Register 4 bit



10. Mux_2_way_4bit

- Design Source VHDL Code of Mux_2_way_4bit

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity Mux_2way_4bit is
    Port ( Sel : in STD_LOGIC;
          A : in STD_LOGIC_VECTOR (3 downto 0);
          B : in STD_LOGIC_VECTOR (3 downto 0);
          Mux_out : out STD_LOGIC_VECTOR (3 downto 0));
end Mux_2way_4bit;


architecture Behavioral of Mux_2way_4bit is

begin
    --Sel=0 for A, Sel=1 for B

    Mux_out(0) <= (A(0) AND (NOT Sel)) or (B(0) AND Sel);
    Mux_out(1) <= (A(1) AND (NOT Sel)) or (B(1) AND Sel);
    Mux_out(2) <= (A(2) AND (NOT Sel)) or (B(2) AND Sel);
    Mux_out(3) <= (A(3) AND (NOT Sel)) or (B(3) AND Sel);

end Behavioral;
```

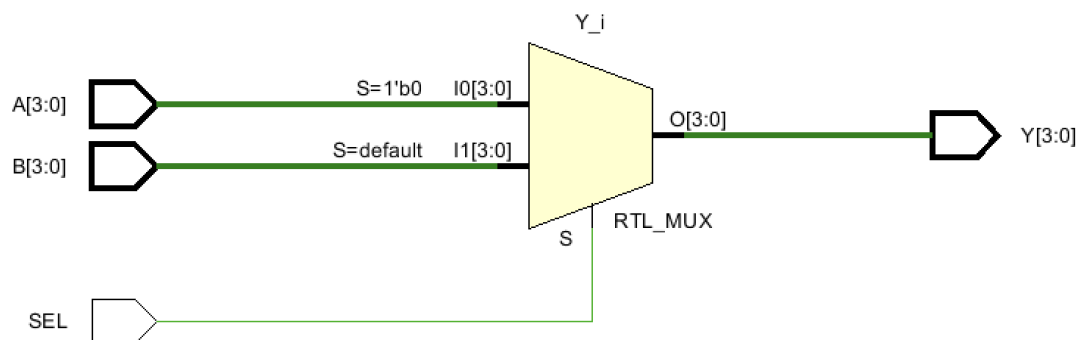- RTL Schematic Diagram of the MUX_2_way_4bit



- Behavioral Simulation Code for MUX_2_way_4bit

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity TB_Mux_2way_4bit is
end TB_Mux_2way_4bit;

architecture Behavioral of TB_Mux_2way_4bit is

    -- Component declaration
    component Mux_2way_4bit is
        Port (
            A   : in  STD_LOGIC_VECTOR(3 downto 0);
            B   : in  STD_LOGIC_VECTOR(3 downto 0);
            SEL : in  STD_LOGIC;
            Y   : out STD_LOGIC_VECTOR(3 downto 0)
        );
    end component;

    -- Testbench signals
    signal A_tb, B_tb, Y_tb : STD_LOGIC_VECTOR(3 downto 0);
    signal SEL_tb : STD_LOGIC;

begin

    -- Instantiate the Unit Under Test (UUT)
    UUT: Mux_2way_4bit
        port map (
            A   => A_tb,
            B   => B_tb,
            SEL => SEL_tb,
            Y   => Y_tb
        );

    -- Stimulus process
    process
    begin
        -- Test case 1: SEL = 0, Y should be A
        A_tb <= "1010";
        B_tb <= "0111";
        SEL_tb <= '0';
        wait for 100 ns;

        -- Test case 2: SEL = 1, Y should be B
        SEL_tb <= '1';
        wait for 100 ns;


        -- Test case 3: Change inputs
        A_tb <= "0001";
        B_tb <= "1111";
        SEL_tb <= '0';
        wait for 100 ns;

        SEL_tb <= '1';
        wait for 100 ns;

        -- Finish
        wait;
    end process;

end Behavioral;
```

● Timing Diagram for MUX_2_way_4bit

 

11. Mux_8_way_4bit

- Design Source VHDL Code of Mux_8_way_4bit

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity Mux_8way_4bit is
    Port ( S : in STD_LOGIC_VECTOR (2 downto 0);
          L0 : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit Input Line 0
          L1 : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit Input Line 1
          L2 : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit Input Line 2
          L3 : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit Input Line 3
          L4 : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit Input Line 4
          L5 : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit Input Line 5
          L6 : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit Input Line 6
          L7 : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit Input Line 7
          EN : in STD_LOGIC;
          OL : out STD_LOGIC_VECTOR (3 downto 0)); -- 4-bit output line
end Mux_8way_4bit;

architecture Behavioral of Mux_8way_4bit is

    component Mux_8_to_1 is
        Port ( S : in STD_LOGIC_VECTOR (2 downto 0);
              D : in STD_LOGIC_VECTOR (7 downto 0);
              EN : in STD_LOGIC;
              Y : out STD_LOGIC);
    end component;

    signal D0 : STD_LOGIC_VECTOR (7 downto 0);
    signal D1 : STD_LOGIC_VECTOR (7 downto 0);
    signal D2 : STD_LOGIC_VECTOR (7 downto 0);
    signal D3 : STD_LOGIC_VECTOR (7 downto 0);

begin

    D0 <= L7(0) & L6(0) & L5(0) & L4(0) & L3(0) & L2(0) & L1(0) & L0(0);
    D1 <= L7(1) & L6(1) & L5(1) & L4(1) & L3(1) & L2(1) & L1(1) & L0(1);
    D2 <= L7(2) & L6(2) & L5(2) & L4(2) & L3(2) & L2(2) & L1(2) & L0(2);
    D3 <= L7(3) & L6(3) & L5(3) & L4(3) & L3(3) & L2(3) & L1(3) & L0(3);

    Mux_0 : Mux_8_to_1
        port map(
            S => S,
            D => D0,
            EN => EN,
            Y => OL(0));

    Mux_1 : Mux_8_to_1
        port map(
            S => S,
            D => D1,
            EN => EN,
            Y => OL(1));

    Mux_2 : Mux_8_to_1
        port map(
            S => S,
            D => D2,
            EN => EN,
            Y => OL(2));


    Mux_3 : Mux_8_to_1
        port map(
            S => S,
            D => D3,
```

```

        EN => EN,
        Y => OL(3));
end Behavioral;

```

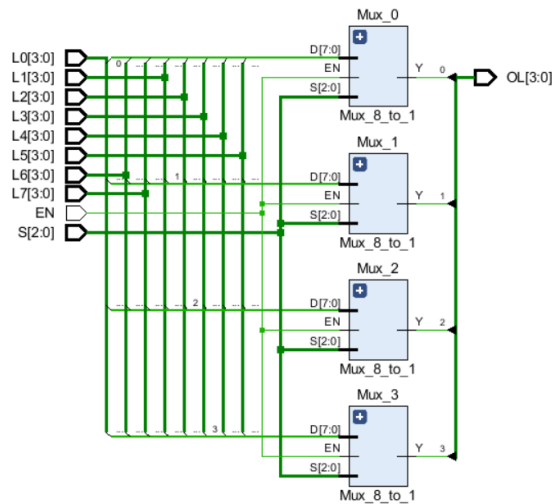- RTL Schematic Diagram of the MUX_8_way_4bit



- Behavioral Simulation Code for MUX_8_way_4bit

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_Mux_8way_4bit is
end TB_Mux_8way_4bit;

architecture Behavioral of TB_Mux_8way_4bit is

    component Mux_8way_4bit is
        Port (
            S : in STD_LOGIC_VECTOR (2 downto 0);
            L0 : in STD_LOGIC_VECTOR (3 downto 0);
            L1 : in STD_LOGIC_VECTOR (3 downto 0);
            L2 : in STD_LOGIC_VECTOR (3 downto 0);
            L3 : in STD_LOGIC_VECTOR (3 downto 0);
            L4 : in STD_LOGIC_VECTOR (3 downto 0);
            L5 : in STD_LOGIC_VECTOR (3 downto 0);
            L6 : in STD_LOGIC_VECTOR (3 downto 0);
            L7 : in STD_LOGIC_VECTOR (3 downto 0);
            EN : in STD_LOGIC;
            OL : out STD_LOGIC_VECTOR (3 downto 0)
        );
    end component;

    signal SEL_tb : std_logic_vector(2 downto 0);
    signal L0_tb, L1_tb, L2_tb, L3_tb, L4_tb, L5_tb, L6_tb, L7_tb : std_logic_vector(3 downto 0);
    signal EN_tb : std_logic := '1'; -- Enable signal set to '1'
    signal OL_tb : std_logic_vector(3 downto 0);

begin

    UUT: Mux_8way_4bit
        port map(
            L0 => L0_tb,
            L1 => L1_tb,
            L2 => L2_tb,
            L3 => L3_tb,
            L4 => L4_tb,
            L5 => L5_tb,
            L6 => L6_tb,
            L7 => L7_tb,

```

```

        S => SEL_tb,
        EN => EN_tb,
        OL => OL_tb
    );

    -- Stimulus process
    process
    begin
        -- Initialize inputs
        L0_tb <= "0100";
        L1_tb <= "0011";
        L2_tb <= "1010";
        L3_tb <= "1011";
        L4_tb <= "1100";
        L5_tb <= "0101";
        L6_tb <= "0110";
        L7_tb <= "1111";

        EN_tb <= '1'; -- Enable the multiplexer

        SEL_tb <= "000";
        wait for 100 ns;

        SEL_tb <= "001";
        wait for 100 ns;

        SEL_tb <= "010";
        wait for 100 ns;

        SEL_tb <= "011";
        wait for 100 ns;

        SEL_tb <= "100";
        wait for 100 ns;

        SEL_tb <= "101";
        wait for 100 ns;

        SEL_tb <= "110";
        wait for 100 ns;


        SEL_tb <= "111";
        wait for 100 ns;

        wait;
    end process;

end Behavioral;

```

- Timing Diagram for MUX_8_way_4bit

 

12. Slow_Clk

- Design Source VHDL Code of Slow_Clk


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
entity Slow_Clk is
    Port ( Clk_in : in STD_LOGIC;
           Clk_out : out STD_LOGIC);
end Slow_Clk;
architecture Behavioral of Slow_Clk is

    signal count: unsigned(27 downto 0) := (others => '0'); --28 bit counter
    --signal clk_status: std_logic := '0';

begin

    process (Clk_in) begin
        if (rising_edge (Clk_in)) then
            count <= count+1;
            Clk_out <= count(27);
            --for simulation use count(2) => output clock frequency = 1/4 *original
            clk frequency
            --Basys board use count(27) => clk_out will change for every
            134,217,728 clk cycles
            --which means slow clk cycle is ~2.685 seconds , frequency is ~0.3725
            Hz
        end if;
    end process;
end Behavioral;
```

- RTL Schematic Diagram of the Slow_Clk

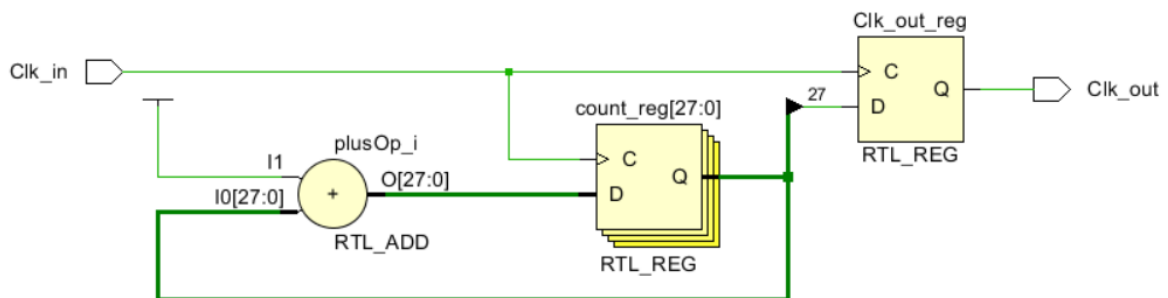

- Behavioral Simulation Code for Slow_Clk

```
entity Slow_Clk_Sim is
-- Port ( );
end Slow_Clk_Sim;

architecture Behavioral of Slow_Clk_Sim is

-- Component Declaration
component Slow_Clk
  Port ( Clk_in : in STD_LOGIC;
         Clk_out : out STD_LOGIC);
end component;

-- Testbench Signals

signal Clk_in : STD_LOGIC:= '0' ;
signal Clk_out : STD_LOGIC;


begin

-- Instantiate the Unit Under Test (UUT)
uut: Slow_Clk
  Port map (
    Clk_in => Clk_in,
    Clk_out => Clk_out
  );

-- Generate 5 rising edges (5 clock cycles)
Clock_process: process
begin
  Clk_in <= not Clk_in;
  wait for 5 ns; -- 10ns full period = 100 MHz
end process;

end Behavioral;
```

- Timing Diagram for slow clock

 

13. Constraint File

```
level signal names in the project

## Clock signal
set_property PACKAGE_PIN W5 [get_ports {Clock}]
    set_property IOSTANDARD LVCMOS33 [get_ports {Clock}]
    create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports {Clock}]

## LEDs
set_property PACKAGE_PIN U16 [get_ports {R7_LED[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {R7_LED[0]}]
set_property PACKAGE_PIN E19 [get_ports {R7_LED[1]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {R7_LED[1]}]
set_property PACKAGE_PIN U19 [get_ports {R7_LED[2]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {R7_LED[2]}]
set_property PACKAGE_PIN V19 [get_ports {R7_LED[3]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {R7_LED[3]}]
set_property PACKAGE_PIN P1 [get_ports {Zero_LED}]
    set_property IOSTANDARD LVCMOS33 [get_ports {Zero_LED}]
set_property PACKAGE_PIN L1 [get_ports {Over_F_LED}]
    set_property IOSTANDARD LVCMOS33 [get_ports {Over_F_LED}]

##7 segment display
set_property PACKAGE_PIN W7 [get_ports {R7_7seg[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {R7_7seg[0]}]
set_property PACKAGE_PIN W6 [get_ports {R7_7seg[1]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {R7_7seg[1]}]
set_property PACKAGE_PIN U8 [get_ports {R7_7seg[2]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {R7_7seg[2]}]
set_property PACKAGE_PIN V8 [get_ports {R7_7seg[3]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {R7_7seg[3]}]
set_property PACKAGE_PIN U5 [get_ports {R7_7seg[4]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {R7_7seg[4]}]
set_property PACKAGE_PIN V5 [get_ports {R7_7seg[5]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {R7_7seg[5]}]
set_property PACKAGE_PIN U7 [get_ports {R7_7seg[6]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {R7_7seg[6]}]

#set_property PACKAGE_PIN V7 [get_ports dp]
    #set_property IOSTANDARD LVCMOS33 [get_ports dp]

set_property PACKAGE_PIN U2 [get_ports {Anode[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {Anode[0]}]
set_property PACKAGE_PIN U4 [get_ports {Anode[1]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {Anode[1]}]
set_property PACKAGE_PIN V4 [get_ports {Anode[2]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {Anode[2]}]
set_property PACKAGE_PIN W4 [get_ports {Anode[3]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {Anode[3]}]

##Buttons
set_property PACKAGE_PIN U18 [get_ports {Reset}]
    set_property IOSTANDARD LVCMOS33 [get_ports {Reset}]
```

◆ Resource Utilization

Name	Slice LUTs (20800)	Slice Registers (41600)	Slice (8150)	LUT as Logic (20800)	LUT Flip Flop Pairs (20800)	Bonded IOB (106)	BUFGCTRL (32)	
▼ N Nanoprocessor	34	60	22	34	11	19	1	
Flag_Register_0 (Flag...	0	2	1	0	0	0	0	
Instruction_Decoder_...	2	14	7	2	1	0	0	
Program_Counter_0 (...)	11	3	5	11	3	0	0	
> Register_Bank_0 (Reg...	20	12	8	20	0	0	0	
SlowClock (Slow_Clk)	1	29	8	1	1	0	0	

2) Design with extended qualifications

◆ Executable Instruction Set

Instruction	Description	Format (17-bit instruction)
MOVI R, d	Move immediate value d to register R, i.e., $R \leftarrow d$, $R \in [0, 7]$, $d \in [0, 255]$	0 1 0 R R R 0 0 0 d d d d d d d
ADD Ra, Rb	Add values in registers Ra and Rb and store the result in Ra, i.e., $Ra \leftarrow Ra + Rb$, $Ra, Rb \in [0, 7]$	0 0 0 Ra Ra Ra Rb Rb Rb 00000000
NEG R	2's complement of registers R, i.e., $R \leftarrow -R$, $R \in [0, 7]$	0 0 1 R R R 000 0 0 0 0 0 0 0
JZR R, d	Jump if value in register R is 0, i.e., If $R == 0$ $PC \leftarrow d$; Else $PC \leftarrow PC + 1$; $R \in [0, 7]$, $d \in [0, 15]$	0 1 1 R R R 0 0 0 0 0 0 0 d d d d
MUL Ra, Rb	Multiply values in registers Ra and Rb and store the result in Ra, i.e., $Ra \leftarrow Ra \times Rb$ $Ra, Rb \in [0, 127]$ (2's complement positive numbers only)	1 0 0 Ra Ra Ra Rb Rb Rb 00000000
JUMP d	Jump to the address d $d \in [0, 15]$	1 0 1 0 0 0 0 0 0 0 0 0 0 d d d d
JNZ R, d	Jump if value in register R is not 0, i.e., If $R \neq 0$ $PC \leftarrow d$; Else $PC \leftarrow PC + 1$; $R \in [0, 7]$, $d \in [0, 15]$	1 1 0 R R R 0 0 0 0 0 0 0 d d d d
COPY Ra Rb	Copy the value in Rb to Ra $Ra \leftarrow Rb$; $R \in [0, 7]$	1 1 1 Ra Ra Ra Rb Rb Rb 00000000

◆ Design Components

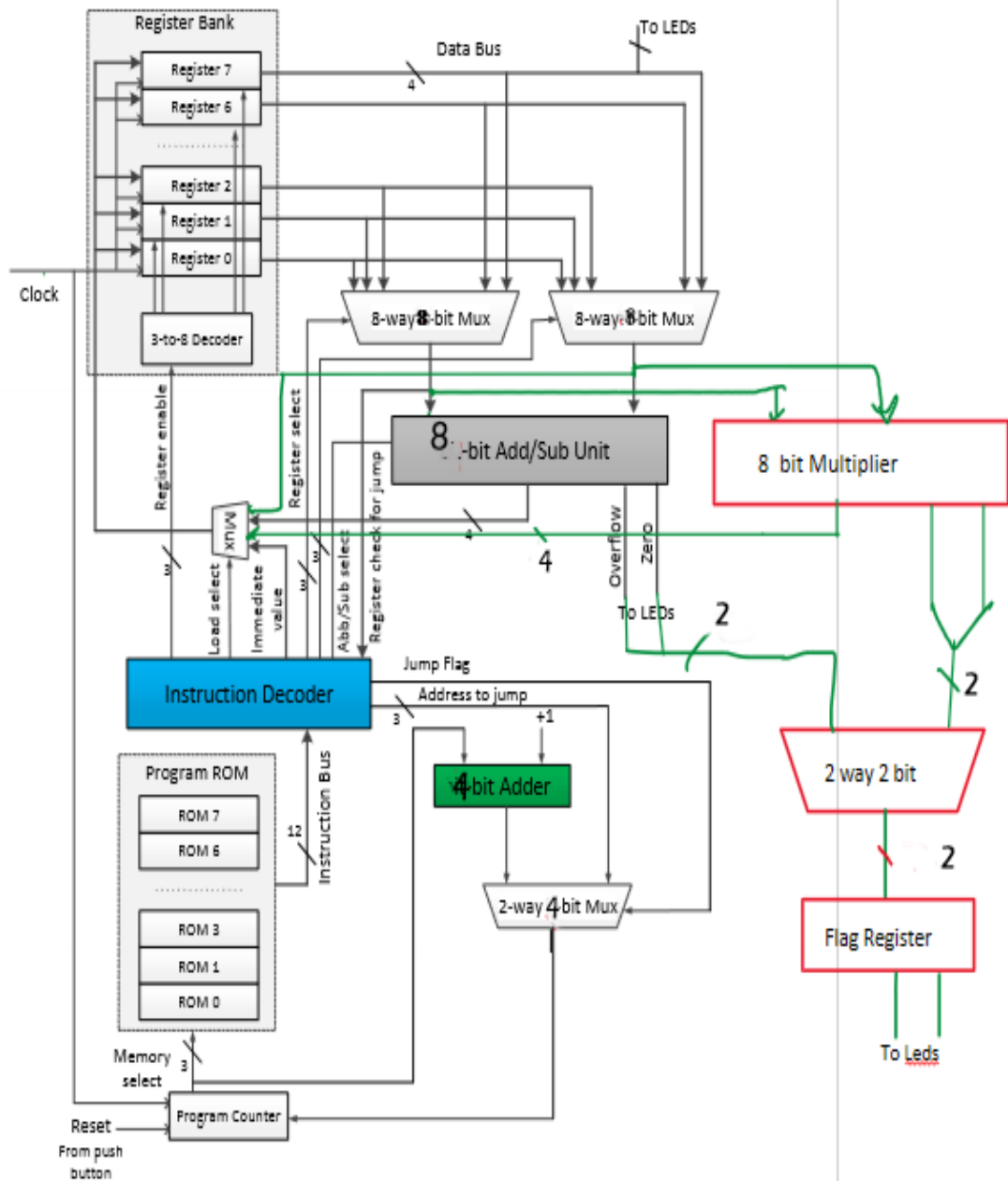


Figure 1 – High-level diagram of the nanoprocessor.

1. Improved Nano Processor

- Design Source VHDL Code of improved Nano Processor

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- arithmetic functions with Signed or Unsigned values
use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity NanoProcessor_Improved is
    Port ( Reset : in STD_LOGIC;
          Clock : in STD_LOGIC;
          R7_LED : out STD_LOGIC_VECTOR (7 downto 0);
          Zero_LED : out STD_LOGIC;
          Over_F_LED : out STD_LOGIC;
          Anode : out STD_LOGIC_VECTOR (3 downto 0);
          R7_7seg : out STD_LOGIC_VECTOR (6 downto 0));
end NanoProcessor_Improved;

architecture Behavioral of NanoProcessor_Improved is

    ----- Components -----

    ----- Slow Clock >>>> Slowed Clock signal so easy to observe -----
    component Slow_Clk is
        Port ( Clk_in : in STD_LOGIC;
              Clk_out : out STD_LOGIC);
    end component;

    -----Instruction Decoder-----
    component Instruction_Decoder is
        Port ( Instruction : in STD_LOGIC_VECTOR (16 downto 0);
              Jump_reg_val : in STD_LOGIC_VECTOR (7 downto 0); --register value for jump check
              Reg_Sel_A : out STD_LOGIC_VECTOR (2 downto 0); --Mux Select signal
              Reg_Sel_B : out STD_LOGIC_VECTOR (2 downto 0); --Muc Selct signal
              Reg_En : out STD_LOGIC_VECTOR (2 downto 0); --Register Bank write enable signal
              Flag_Reg_En : out STD_LOGIC; -- Enable for ADD_SUB_Units and Multiplier Flag
              Flag_Reg_Input_Sel : out STD_LOGIC; -- 0 for ADD_SUB_unit ,1 for multiplier
              Jump_Address : out STD_LOGIC_VECTOR (3 downto 0);
              Jump_Flag : out STD_LOGIC;
              Add_Sub_Sel : out STD_LOGIC; -- 0 for add , 1 for subtract
              Load_Sel : out STD_LOGIC_VECTOR (1 downto 0); -- 00 for immediarte value, 01 for add_sub
              unit value
              Immediate_Value : out STD_LOGIC_VECTOR (7 downto 0));
    end component;

    ----- Register Bank (8 8-bit registers) -----
    component Reg_Bank is
        Port ( RegSel : in STD_LOGIC_VECTOR (2 downto 0); --Register Select signal
              D : in STD_LOGIC_VECTOR (7 downto 0); --Data line
              Reset : in STD_LOGIC;
              Clk : in STD_LOGIC;
              R0 : out STD_LOGIC_VECTOR (7 downto 0);
              R1 : out STD_LOGIC_VECTOR (7 downto 0);
              R2 : out STD_LOGIC_VECTOR (7 downto 0);
              R3 : out STD_LOGIC_VECTOR (7 downto 0);
              R4 : out STD_LOGIC_VECTOR (7 downto 0);
              R5 : out STD_LOGIC_VECTOR (7 downto 0);
              R6 : out STD_LOGIC_VECTOR (7 downto 0);
              R7 : out STD_LOGIC_VECTOR (7 downto 0));
    end component;
```

```

---- Flag Register (Zero, Overflow) -----
component Flag_register is
  Port ( Zero : in STD_LOGIC;    --zero signal from ADD_SUB_Unit
        Over_f : in STD_LOGIC;  --overflow signal from ADD_SUB_Unit
        En : in STD_LOGIC;
        reset : in STD_LOGIC;
        Clk : in STD_LOGIC;
        Zero_Flag : out STD_LOGIC;
        OverFlow_Flag : out STD_LOGIC);
end component;

---- Program Counter (register) -----
component Program_Counter is
  Port ( D : in STD_LOGIC_VECTOR (3 downto 0);
        Reset : in STD_LOGIC;
        Clk : in STD_LOGIC;
        P_count : out STD_LOGIC_VECTOR (3 downto 0));
end component;

---- 8-bit ADD_SUB_Unit -----
component ADD_SUB_8bit is
  Port ( Ins : in STD_LOGIC; -- instruction (ADD =0, SUB = 1) (also works as C_in)
        A : in STD_LOGIC_VECTOR (7 DOWNTO 0);
        B : in STD_LOGIC_VECTOR (7 DOWNTO 0);
        S : out STD_LOGIC_VECTOR (7 DOWNTO 0);
        Q_flow : out STD_LOGIC;
        Zero: out STD_LOGIC);
end component;

---- 8 bit Multiplier -----
component Multiplier_8bit is
  Port ( A : in STD_LOGIC_VECTOR (7 downto 0);
        B : in STD_LOGIC_VECTOR (7 downto 0);
        Ans : out STD_LOGIC_VECTOR (7 downto 0);
        Over_f : out STD_LOGIC;
        Zero : out STD_LOGIC);
end component;

---- 4-bit RCA --(Adder)-----
component RCA_4bit is
  Port (
    A : in STD_LOGIC_VECTOR (3 DOWNTO 0);
    B : in STD_LOGIC_VECTOR (3 DOWNTO 0);
    S : out STD_LOGIC_VECTOR (3 DOWNTO 0);
    C_in :in STD_LOGIC;
    C_out: out STD_LOGIC);
end component;

---- 8 way 8-bit Multiplexer -----
component Mux_8way_8bit is
  Port (
    D0, D1, D2, D3 : in  STD_LOGIC_VECTOR(7 downto 0);
    D4, D5, D6, D7 : in  STD_LOGIC_VECTOR(7 downto 0);
    SEL              : in  STD_LOGIC_VECTOR(2 downto 0); -- 3-bit selection
    Y                : out STD_LOGIC_VECTOR(7 downto 0)  -- 8-bit output
  );
end component;

---- 4 way 8-bit Multiplexer -----
component Mux_4way_8bit is
  Port (
    D0, D1, D2, D3 : in  STD_LOGIC_VECTOR(7 downto 0);
    SEL              : in  STD_LOGIC_VECTOR(1 downto 0); -- 2-bit selection
    Y                : out STD_LOGIC_VECTOR(7 downto 0)  -- 8-bit output
  );
end component;

---- 2 way 4-bit Multiplexer -----
component Mux_2way_4bit is
  Port (
    A : in  STD_LOGIC_VECTOR(3 downto 0); -- 4-bit input A
    B : in  STD_LOGIC_VECTOR(3 downto 0); -- 4-bit input B
    SEL : in  STD_LOGIC;                  -- Selection line
    Y : out STD_LOGIC_VECTOR(3 downto 0)  -- 4-bit output
  );
end component;

```



```

    );
end component;

---- 2 way 2-bit Multiplexer -----
component Mux_2way_2bit is
    Port ( A : in STD_LOGIC_VECTOR (1 downto 0);
          B : in STD_LOGIC_VECTOR (1 downto 0);
          SEL: in STD_LOGIC;
          Y : out STD_LOGIC_VECTOR (1 downto 0));
end component;

----- Program ROM >>>> Stored Machine language Assembly code -----
component Program_ROM is
    Port ( address : in STD_LOGIC_VECTOR (3 downto 0);
          data : out STD_LOGIC_VECTOR (16 downto 0));
end component;

---- 7 Segment display outputs setup----
component Display_7seg_out is
    Port ( Number : in STD_LOGIC_VECTOR (7 downto 0);
          Clock : in STD_LOGIC;
          Cathode : out STD_LOGIC_VECTOR (6 downto 0);
          Anode : out STD_LOGIC_VECTOR (3 downto 0));
end component;

-----Signals-----
signal Slow_clock :std_logic;
signal instruction : std_logic_vector (16 downto 0);
signal Mux_A_out ,Mux_B_out : std_logic_vector (7 downto 0); -- 8way MUX outputs
signal Mux_A_Sel, Mux_B_Sel : std_logic_vector (2 downto 0); -- 8way MUX Select signal
signal Reg_EN : std_logic_vector (2 downto 0); -- Register bank select reg for write enable signal
signal Flag_Reg_EN : std_logic; --flag register enable signal
signal Flag_Reg_Input_Sel: std_logic;
signal Address_to_jump : std_logic_vector (3 downto 0);
signal Jump_Flag : std_logic;
signal Add_Sub_Sel : std_logic;
signal Load_Sel : std_logic_vector (1 downto 0); -- load select for register write data bus
signal Immediate_Value: std_logic_vector (7 downto 0);

signal Reg_Data_in: std_logic_vector (7 downto 0); --Register Data in Bus
--Register Data outs
signal Reg_0, Reg_1, Reg_2, Reg_3, Reg_4, Reg_5, Reg_6, Reg_7: std_logic_vector (7 downto 0);
signal Add_Sub_Out : std_logic_vector (7 downto 0);
signal Multiplier_Out : std_logic_vector (7 downto 0);
signal Flag_reg_in_2bit : std_logic_vector (1 downto 0);
signal adder_0_flow_Zero : std_logic_vector (1 downto 0);
signal mul_0_flow_Zero : std_logic_vector (1 downto 0);
signal 0_flow_Zero : std_logic_vector (1 downto 0);

signal Program_C_in, Program_C_out: std_logic_vector (3 downto 0);
signal Program_C_Incrementer_out : std_logic_vector (3 downto 0);

begin

    SlowClock : Slow_Clk
        port map(
            Clk_in => Clock,
            Clk_out => Slow_clock );

    Instruction_Decoder_0: Instruction_Decoder
        port map(
            Instruction      => instruction,
            Jump_reg_val     => Mux_A_out,
            Reg_Sel_A        => Mux_A_Sel,
            Reg_Sel_B        => Mux_B_Sel,
            Reg_En           => Reg_EN,
            Flag_Reg_En      => Flag_Reg_EN,
            Flag_Reg_Input_Sel => Flag_Reg_Input_Sel,
            Jump_Address     => Address_to_jump,
            Jump_Flag        => Jump_Flag,
            Add_Sub_Sel      => Add_Sub_Sel,
            Load_Sel        => Load_Sel,
            Immediate_Value  => Immediate_Value);

```

```

Register_Bank_0 : Reg_Bank
  port map(
    RegSel  => Reg_EN,
    D       => Reg_Data_in,
    Reset   => Reset,
    Clk     => Slow_clock,
    R0      => Reg_0,
    R1      => Reg_1,
    R2      => Reg_2,
    R3      => Reg_3,
    R4      => Reg_4,
    R5      => Reg_5,
    R6      => Reg_6,
    R7      => Reg_7);

Mux_8way_8bit_A: Mux_8way_8bit
  port map(
    D0  => Reg_0,
    D1  => Reg_1,
    D2  => Reg_2,
    D3  => Reg_3,
    D4  => Reg_4,
    D5  => Reg_5,
    D6  => Reg_6,
    D7  => Reg_7,
    SEL => Mux_A_Sel,
    Y   => Mux_A_out);

Mux_8way_8bit_B: Mux_8way_8bit
  port map(
    D0  => Reg_0,
    D1  => Reg_1,
    D2  => Reg_2,
    D3  => Reg_3,
    D4  => Reg_4,
    D5  => Reg_5,
    D6  => Reg_6,
    D7  => Reg_7,
    SEL => Mux_B_Sel,
    Y   => Mux_B_out);

ADD_SUB_UNIT: Add_Sub_8bit
  port map(
    Ins => Add_Sub_Sel,
    A   => Mux_A_out,
    B   => Mux_B_out,
    S   => Add_Sub_Out,
    O_flow => adder_0_flow_Zero(1),
    Zero  => adder_0_flow_Zero(0));

Multiplier_8_0: Multiplier_8bit
  Port map(
    A => Mux_A_out,
    B => Mux_B_out,
    Ans => Multiplier_Out,
    Over_f => mul_0_flow_Zero(1),
    Zero => mul_0_flow_Zero(0));

Mux_for_Reg_Write_Data_Bus: Mux_4way_8bit
  port map(
    D0  => Immediate_Value,
    D1  => Add_Sub_Out,
    D2  => Multiplier_Out,
    D3  => Mux_B_out,
    SEL => Load_Sel,
    Y   => Reg_Data_in);

Flag_input_select :Mux_2way_2bit
  port map(
    A  => adder_0_flow_Zero,
    B  => mul_0_flow_Zero,

```

```

        SEL => Flag_Reg_Input_Sel,
        Y  => O_flow_Zero);

Flag_Register_0 :Flag_register
port map(
    Zero    => O_flow_Zero(0),
    Over_f  => O_flow_Zero(1),
    En      => Flag_Reg_EN,
    reset   => Reset,
    Clk     => Slow_clock,
    Zero_Flag => Zero_LED,
    Overflow_Flag => Over_F_LED);

Program_Counter_0: Program_Counter
port map(
    D      => Program_C_in,
    Reset  => Reset,
    Clk    => Slow_clock,
    P_count => Program_C_out);

Program_Count_Incrementer: RCA_4bit
port map(
    A  => Program_C_out,
    B  => "0001",
    C_in => '0',
    S  => Program_C_Incrementer_out,
    C_out => open);

Mux_2way_3bit_0 : Mux_2way_4bit
port map(
    A  => Program_C_Incrementer_out,
    B  => Address_to_jump,
    SEL => Jump_Flag,
    Y  => Program_C_in);

Program_ROM_0: Program_ROM
Port map(
    address => Program_C_out,
    data    => instruction);

---- Output Settings -----
-- Zero and Overflow outputs done in above

--LED output
R7_LED  <= Reg_7;

--7 segmented Display out
Display_7seg_out_0 :Display_7seg_out
port map(
    Number  => Reg_7,
    Clock   => Clock,
    Cathode => R7_7seg,
    Anode   => Anode);

end Behavioral;

```



```
end Behavioral;
```

2. Instruction_Decoder

- Design Source VHDL Code of improved Instruction_Decoder

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity Instruction_Decoder is
    Port ( Instruction : in STD_LOGIC_VECTOR (16 downto 0);
          Jump_reg_val : in STD_LOGIC_VECTOR (7 downto 0); --register value for jump check
          Reg_Sel_A: out STD_LOGIC_VECTOR (2 downto 0);    --Mux Select signal
          Reg_Sel_B: out STD_LOGIC_VECTOR (2 downto 0);    --Mux Select signal
          Reg_En :out STD_LOGIC_VECTOR (2 downto 0);       --Register Bank write enable signal
          Flag_Reg_En : out STD_LOGIC;                    -- Enable for ADD_SUB_Units and Multiplier Flag
          Flag_Reg_Input_Sel: out STD_LOGIC; -- 0 for ADD_SUB_unit ,1 for multiplier
          Jump_Address : out STD_LOGIC_VECTOR (3 downto 0);
          Jump_Flag : out STD_LOGIC;
          Add_Sub_Sel : out STD_LOGIC; -- 0 for add , 1 for subtract
          Load_Sel : out STD_LOGIC_VECTOR (1 downto 0); -- 00 for immediate value, 01 for add_sub
          unit value
          Immediate_Value : out STD_LOGIC_VECTOR (7 downto 0));
end Instruction_Decoder;

architecture Behavioral of Instruction_Decoder is

    --signal Op_code : STD_LOGIC_VECTOR (1 downto 0);

begin

    Process (Instruction, Jump_reg_val)
    begin

        if Instruction (16 downto 14) = "000" then -- ADD
            Jump_Flag <= '0';
            Reg_Sel_A <= Instruction(13 downto 11);
            Reg_Sel_B <= Instruction(10 downto 8);
            Add_Sub_Sel <= '0';
            Load_Sel <= "01";
            Reg_En <= Instruction(13 downto 11);
            Flag_Reg_Input_Sel <= '0';
            Flag_Reg_En <= '1';

        elsif Instruction (16 downto 14) = "001" then -- Neg
            Jump_Flag <= '0';
            Reg_Sel_A <= Instruction(13 downto 11);
            Reg_Sel_B <= Instruction(10 downto 8);
            Add_Sub_Sel <= '1';
            Load_Sel <= "01";
            Reg_En <= Instruction(13 downto 11);
            Flag_Reg_Input_Sel <= '0';
            Flag_Reg_En <= '1';

        elsif Instruction (16 downto 14) = "010" then -- MOVI
            Jump_Flag <= '0';
            Load_Sel <= "00";
            Reg_En <= Instruction(13 downto 11);
            Flag_Reg_En <= '0';
            Immediate_value <= Instruction(7 downto 0);

        --10 for multiplier, 11 for Copy line
    end process;
```

```

elseif Instruction (16 downto 14) = "011" then --JZR (jump if Reg is zero)
    Reg_En <= "000";
    Flag_Reg_En <= '0';
    Reg_Sel_A <= Instruction(13 downto 11);
    if Jump_reg_val ="00000000" then
        Jump_Flag <= '1';
        Jump_Address <= Instruction (3 downto 0);
    else
        Jump_Flag <= '0';
    end if;

elseif Instruction (16 downto 14) = "100" then --MUL
    Jump_Flag <= '0';
    Reg_Sel_A <= Instruction(13 downto 11);
    Reg_Sel_B <= Instruction(10 downto 8);
    Load_Sel <= "10";
    Reg_En <= Instruction(13 downto 11);
    Flag_Reg_Input_Sel <= '1';
    Flag_Reg_En <='1';

elseif Instruction (16 downto 14) = "101" then --JUMP
    Reg_En <= "000";
    Flag_Reg_En <= '0';
    Jump_Flag <= '1';
    Jump_Address <= Instruction (3 downto 0);


elseif Instruction (16 downto 14) = "110" then --JNZ (jump if Reg not zero)
    Reg_En <= "000";
    Flag_Reg_En <= '0';
    Reg_Sel_A <= Instruction(13 downto 11);
    if Jump_reg_val /= "00000000" then
        Jump_Flag <= '1';
        Jump_Address <= Instruction (3 downto 0);
    else
        Jump_Flag <= '0';
    end if;
elseif Instruction (16 downto 14) = "111" then --- COPY (copy reg B to reg A)
    Jump_Flag <= '0';
    Flag_Reg_En <='0';
    Reg_Sel_B <= Instruction(10 downto 8);
    Load_Sel <= "11";
    Reg_En <= Instruction(13 downto 11);

end if;

end process;

```

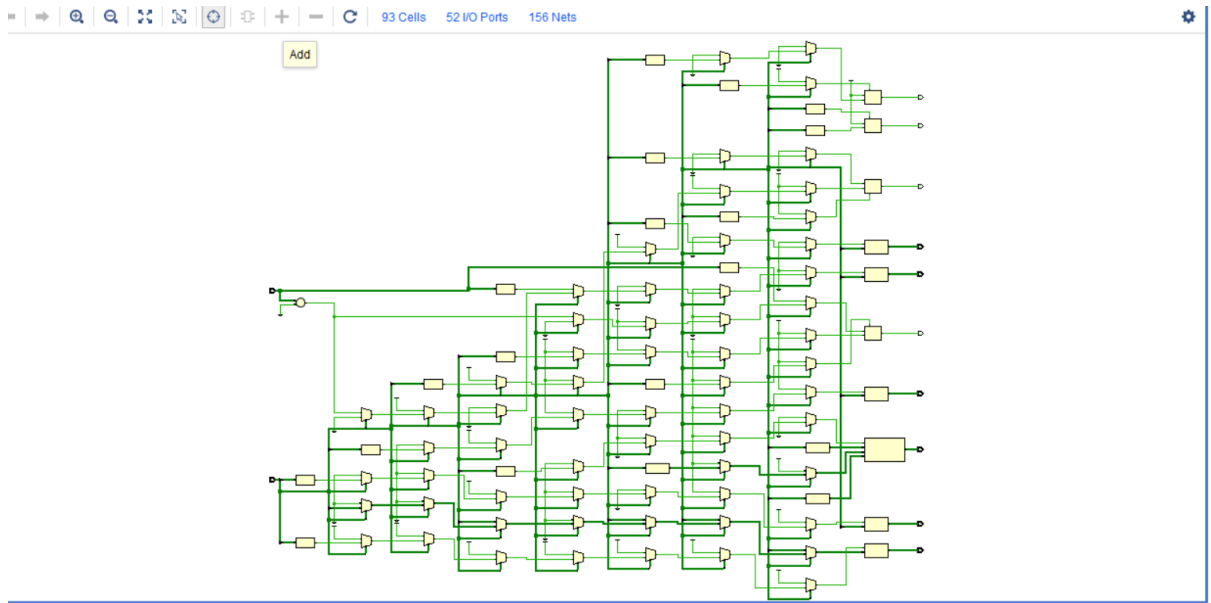- RTL Schematic Diagram of the improved Instruction_Decoder



- Behavioral Simulation Code for improved Instruction_Decoder

```
entity TB_Instruction_Decoder is
-- Port ( );
end TB_Instruction_Decoder;

architecture Behavioral of TB_Instruction_Decoder is

component Instruction_Decoder is
Port ( Instruction : in STD_LOGIC_VECTOR (16 downto 0);
      Jump_reg_val : in STD_LOGIC_VECTOR (7 downto 0); --register value for jump check
      Reg_Sel_A: out STD_LOGIC_VECTOR (2 downto 0); --Mux Select signal
      Reg_Sel_B: out STD_LOGIC_VECTOR (2 downto 0); --Mux Select signal
      Reg_En :out STD_LOGIC_VECTOR (2 downto 0); --Register Bank write enable signal
      Flag_Reg_En : out STD_LOGIC; -- Enable for ADD_SUB_Units and Multiplier Flag
      Flag_Reg_Input_Sel: out STD_LOGIC; -- 0 for ADD_SUB_unit ,1 for multiplier
      Jump_Address : out STD_LOGIC_VECTOR (3 downto 0);
      Jump_Flag : out STD_LOGIC;
      Add_Sub_Sel : out STD_LOGIC; -- 0 for add , 1 for subtract
      Load_Sel : out STD_LOGIC_VECTOR (1 downto 0); -- 00 for immediate value, 01 for add_sub
unit value
--10 for multiplier, 11 for Copy line
      Immediate_Value : out STD_LOGIC_VECTOR (7 downto 0));
end component;

signal Instruction : STD_LOGIC_VECTOR (16 downto 0);
signal Jump_reg_val ,Immediate_Value: STD_LOGIC_VECTOR (7 downto 0);
signal Reg_Sel_A, Reg_Sel_B, Reg_En : STD_LOGIC_VECTOR (2 downto 0);
signal Jump_Address : STD_LOGIC_VECTOR (3 downto 0);
signal Flag_Reg_En,Add_Sub_Sel,Jump_Flag : STD_LOGIC;
signal Load_Sel : STD_LOGIC_VECTOR (1 downto 0);
signal Flag_Reg_Input_Sel: STD_LOGIC;
```



```

begin

    UUT:Instruction_Decoder
        port map (
            Instruction=>Instruction,
            Jump_reg_val=>Jump_reg_val,
            Reg_Sel_A=> Reg_Sel_A,
            Reg_Sel_B=> Reg_Sel_B,
            Reg_En=> Reg_En,
            Flag_Reg_En=>Flag_Reg_En,
            Flag_Reg_Input_Sel => Flag_Reg_Input_Sel,
            Jump_Address=>Jump_Address,
            Jump_Flag=>Jump_Flag,
            Add_Sub_Sel=>Add_Sub_Sel,
            Load_Sel =>Load_Sel ,
            Immediate_Value=>Immediate_Value );

    process
    begin

        Jump_reg_val <= "00000000";

        Instruction <= "000001010000000000";
        wait for 100ns;

        Instruction <= "001101000000000000";
        wait for 100ns;

        Instruction <= "01010000000110110";
        wait for 100ns;

        Instruction <= "01111000000000101"; --JZR
        wait for 100ns;

        Instruction <= "11001100000001001"; --JNZ
        wait for 100ns;

        Jump_reg_val <= "00011101";

        Instruction <= "01111000000000101"; --JZR
        wait for 100ns;

        Instruction <= "11001100000001001"; --JNZ
        wait for 100ns;

        Instruction <= "100100010000000000"; --MUL
        wait for 100ns;


        Instruction <= "111001101000000000"; --COPY
        wait ;

    end process;

end Behavioral;

```

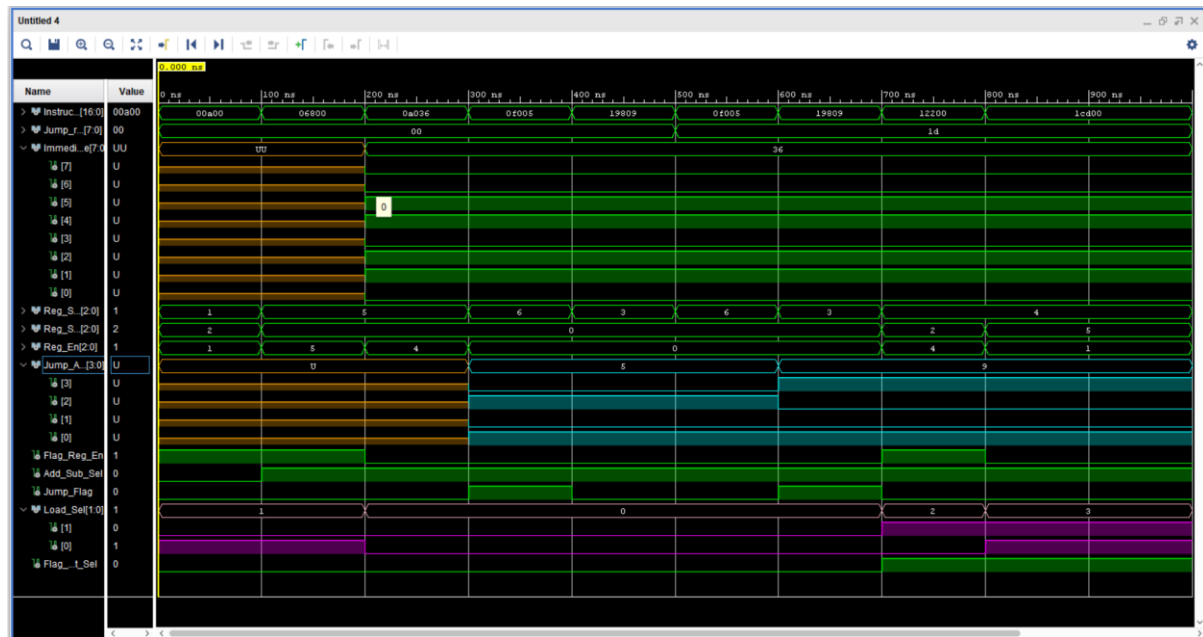- Timing Diagram for improved Instruction_Decoder



3. Add Sub 8bit

- Design Source VHDL Code of improved ADD_SUB_8bit

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity ADD_SUB_8bit is
    Port ( Ins : in STD_LOGIC; -- instruction (ADD =0, SUB = 1) (also works as C_in)
          A : in STD_LOGIC_VECTOR (7 DOWNTO 0);
          B : in STD_LOGIC_VECTOR (7 DOWNTO 0);
          S : out STD_LOGIC_VECTOR (7 DOWNTO 0);
          Q_flow : out STD_LOGIC;
          Zero: out STD_LOGIC);
end ADD_SUB_8bit;

architecture Behavioral of ADD_SUB_8bit is

    component FA is
        Port ( A : in STD_LOGIC;
              B : in STD_LOGIC;
              C_in : in STD_LOGIC;
              S : out STD_LOGIC;
              C_out : out STD_LOGIC);
    end component;

    signal FA0_C, FA1_C, FA2_C, FA3_C, FA4_C, FA5_C, FA6_C, FA7_C : std_logic;
    Signal A0, A1, A2, A3, A4, A5, A6, A7: std_logic;
    Signal S0, S1, S2, S3, S4, S5, S6, S7 : std_logic;

    begin

        -- When Subtracting we will do B-A

        A0 <= A(0) XOR Ins;
        A1 <= A(1) XOR Ins;
        A2 <= A(2) XOR Ins;
        A3 <= A(3) XOR Ins;
        A4 <= A(4) XOR Ins;
        A5 <= A(5) XOR Ins;
        A6 <= A(6) XOR Ins;
        A7 <= A(7) XOR Ins;

        FA_0 : FA
            port map(
                A=>A0,
                B=>B(0),
                C_in=> Ins,
                S=> S0,
                C_out => FA0_C);

        FA_1 : FA
            port map(
                A=>A1,
                B=>B(1),
                C_in=> FA0_C,
                S=> S1,
                C_out => FA1_C);
```

```

FA_2 : FA
  port map(
    A=>A2,
    B=>B(2),
    C_in=> FA1_C,
    S=> S2,
    C_out => FA2_C);

FA_3 : FA
  port map(
    A=>A3,
    B=>B(3),
    C_in=> FA2_C,
    S=> S3,
    C_out => FA3_C);

FA_4 : FA
  port map(
    A=>A4,
    B=>B(4),
    C_in=> FA3_C,
    S=> S4,
    C_out => FA4_C);

FA_5 : FA
  port map(
    A=>A5,
    B=>B(5),
    C_in=> FA4_C,
    S=> S5,
    C_out => FA5_C);

FA_6 : FA
  port map(
    A=>A6,
    B=>B(6),
    C_in=> FA5_C,
    S=> S6,
    C_out => FA6_C);


FA_7 : FA
  port map(
    A=>A7,
    B=>B(7),
    C_in=> FA6_C,
    S=> S7,
    C_out => FA7_C);

S <= S7 & S6 & S5 & S4 & S3 & S2 & S1 & S0;
Zero <= ( (NOT S0) AND (NOT S1) AND (NOT S2) AND (NOT S3)AND (NOT S4) AND (NOT S5) AND (NOT S6) AND
(NOT S7) );
O_Flow <= FA7_C XOR FA6_C;

end Behavioral;

```

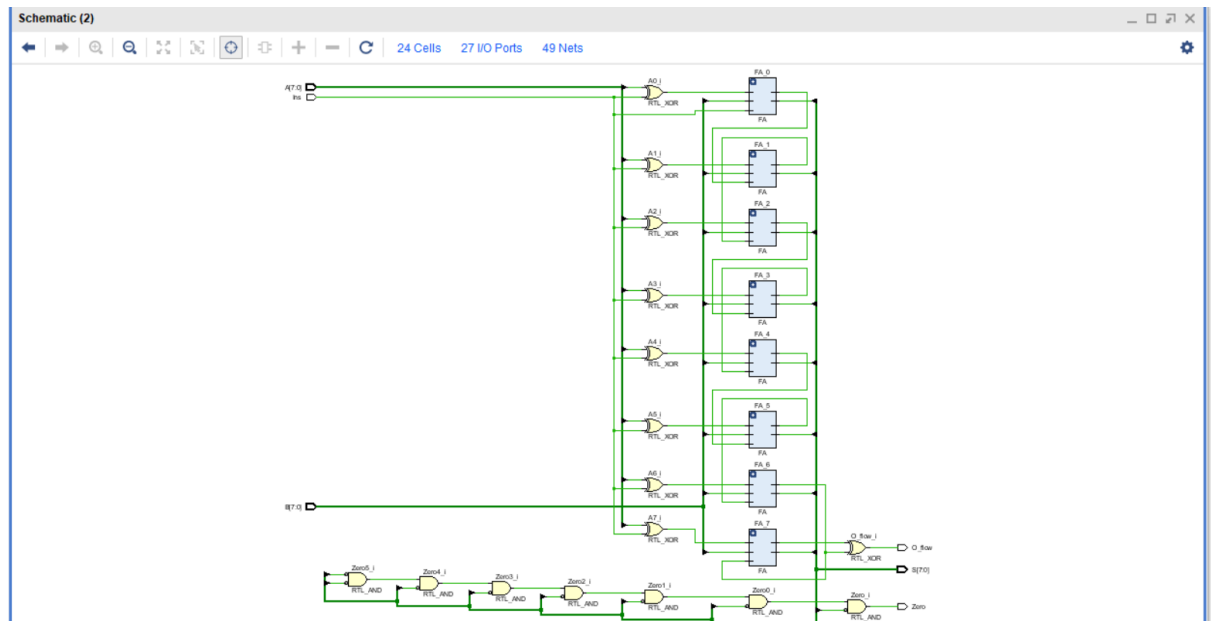- RTL Schematic Diagram of the improved ADD_SUB_8bit



- Behavioral Simulation Code for improved ADD_SUB_8bit

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity TB_ADD_SUB_8bit is
-- Port ( );
end TB_ADD_SUB_8bit;

architecture Behavioral of TB_ADD_SUB_8bit is

component ADD_SUB_8bit is
Port ( Ins : in STD_LOGIC; -- instruction (ADD = 0, SUB = 1) (also works as C_in)
      A : in STD_LOGIC_VECTOR (7 DOWNTO 0);
      B : in STD_LOGIC_VECTOR (7 DOWNTO 0);
      S : out STD_LOGIC_VECTOR (7 DOWNTO 0);
      O_flow : out STD_LOGIC;
      Zero : out STD_LOGIC);
end component;

signal a,b,s : std_logic_vector (7 downto 0);
signal ins, O_f, z :std_logic;

begin

    UTT: ADD_SUB_8bit
    port map(
        Ins => ins,
        A => a,

```

```

B => b,
S => s,
O_flow => O_f,
Zero => z );

process
begin
  a <= "01110010";
  b <= "01100101";
  ins <= '0';
  wait for 100ns;

  ins <= '1';
  wait for 100ns;

  a <= "00110011";
  b <= "01010101";
  ins <= '0';
  wait for 100ns;

  ins <= '1';
  wait for 100ns;

  a <= "00001111";
  b <= "00001111";
  ins <= '0';
  wait for 100ns;

  ins <= '1';
  wait for 100ns;

  a<="01111110";
  b<="00000001";
  ins <= '0';
  wait for 100ns;


  ins <='1';

  wait;

end process;
end Behavioral;

```

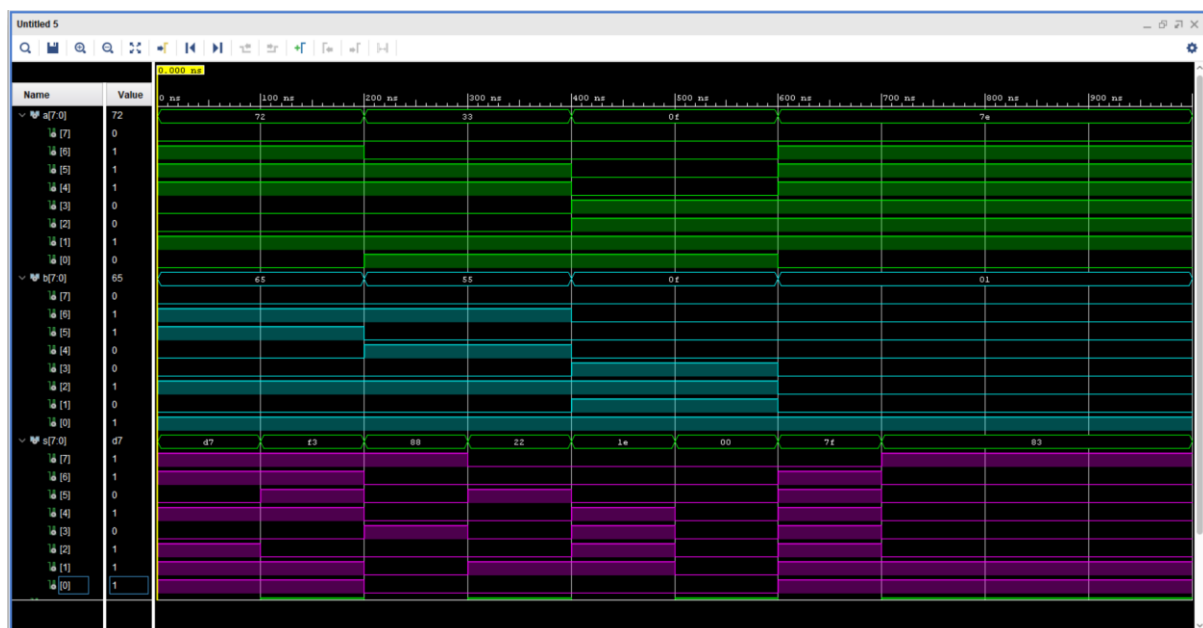- Timing Diagram for improved ADD SUB 8bit



4. Display 7 segment

- Design Source VHDL Code of improved Display_7seg_out

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity Display_7seg_out is
    Port ( Number : in STD_LOGIC_VECTOR (7 downto 0);
          Clock : in STD_LOGIC;
          Cathode : out STD_LOGIC_VECTOR (6 downto 0);
          Anode : out STD_LOGIC_VECTOR (3 downto 0));
end Display_7seg_out;

architecture Behavioral of Display_7seg_out is

    component LUT_16_7seg is
        Port ( value : in STD_LOGIC_VECTOR (7 downto 0);
              data_dis_0 : out STD_LOGIC_VECTOR (6 downto 0);
              data_dis_1 : out STD_LOGIC_VECTOR (6 downto 0);
              data_dis_2 : out STD_LOGIC_VECTOR (6 downto 0));
    end component;

    signal counter : integer:= 0;
    signal disp_ID : unsigned(1 downto 0):= "00";
    signal data_dis_0, data_dis_1, data_dis_2 : STD_LOGIC_VECTOR (6 downto 0);

begin

    process(Clock)
    begin
        if rising_edge(Clock) then
            if counter = 4 then -- ~333 µs at 100 MHz
                counter <= 0;

                -- Cycle digit index 0 -> 1 -> 2 -> 0 ...
                if disp_ID = "10" then
                    disp_ID <= "00";
                else
                    disp_ID <= disp_ID + 1;
                end if;
            else
                counter <= counter + 1;
            end if;
        end if;
    end process;

    LUT_16_7seg_0 : LUT_16_7seg
    port map(
        value => Number,
        data_dis_0 => data_dis_0,
        data_dis_1 => data_dis_1,
        data_dis_2 => data_dis_2);

    process (data_dis_0, data_dis_1, data_dis_2, disp_ID)
    begin
        if disp_ID = "00" then
            Anode <= "1110";
            Cathode <= data_dis_0;

        elsif disp_ID = "01" then
            Anode <= "1101";
```


```

        Cathode <= data_dis_1;

    elsif disp_ID ="10" then
        Anode <= "1011";
        Cathode <= data_dis_2;
    end if;
end process;

end Behavioral;
```

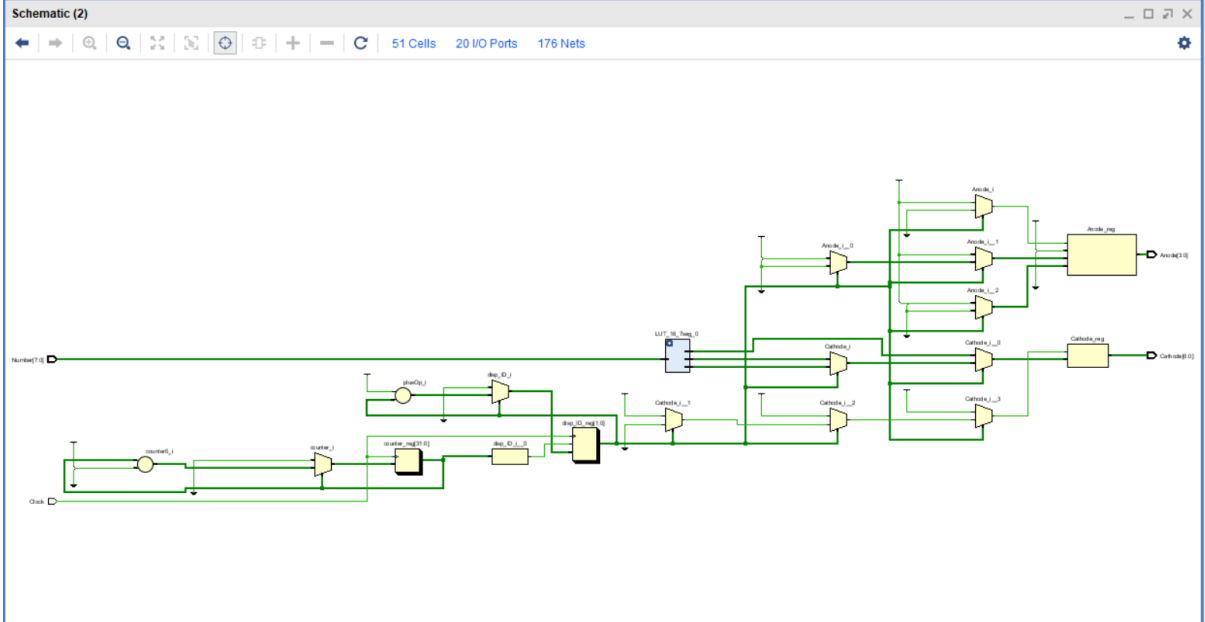- RTL Schematic Diagram of the improved Display_7seg_out



- Behavioral Simulation Code for improved Display 7seg_out

```

entity TB_Display_7seg_out is
    -- Port ( );
end TB_Display_7seg_out;

architecture Behavioral of TB_Display_7seg_out is

    component Display_7seg_out is
        Port ( Number : in STD_LOGIC_VECTOR (7 downto 0);
              Clock : in STD_LOGIC;
              Cathode : out STD_LOGIC_VECTOR (6 downto 0);
              Anode : out STD_LOGIC_VECTOR (3 downto 0));
    end component;

    signal number : STD_LOGIC_VECTOR (7 downto 0);
    signal clk : STD_LOGIC := '0';
    signal cathode: STD_LOGIC_VECTOR (6 downto 0);
    signal anode : STD_LOGIC_VECTOR (3 downto 0);

begin

    process
    begin
        clk <= not clk;
        wait for 2 ns;
    end process;

    UUT:Display_7seg_out
    port map(
        Number => number,
        Clock => clk,
        Cathode => cathode,

```



```

        Anode    => anode);

process
begin
    number <= "00010001";
    wait for 150ns;

    number <= "11101100";
    wait for 150ns;

    number <= "01110001";
    wait for 150ns;

    number <= "00110000";
    wait for 150ns;

    number <= "00000000";
    --    wait for 150ns;


    --    number <= "10011001";
    --    wait for 150ns;

    --    number <= "11111111";
    wait;
end process;

end Behavioral;

```

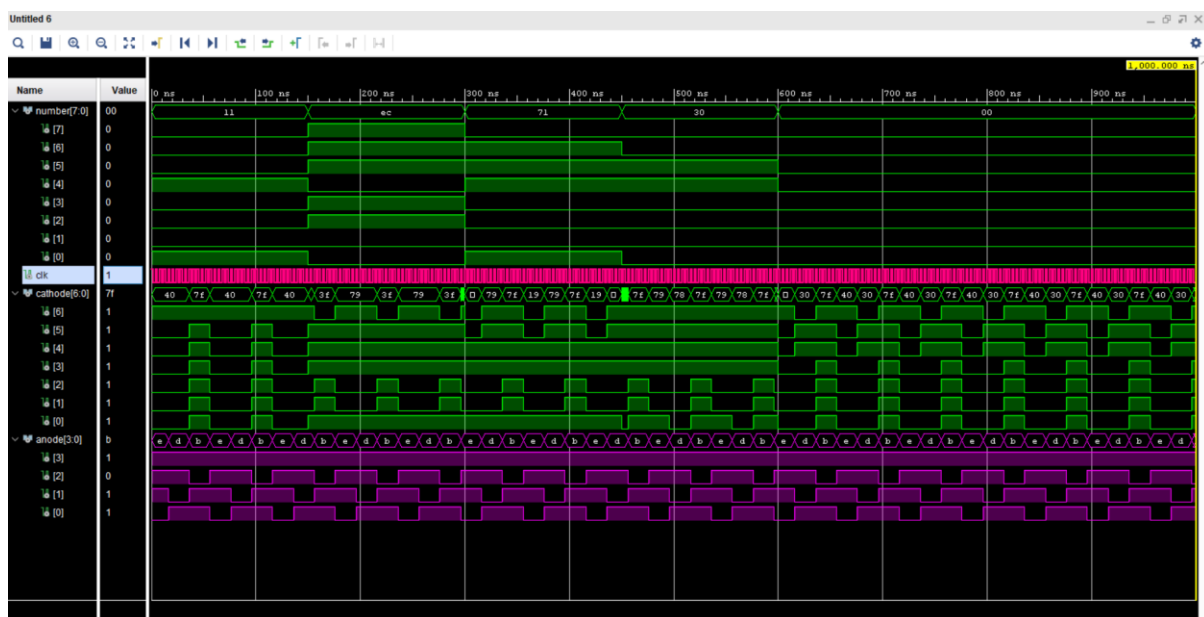- Timing Diagram for improved Display 7seg_out



5. Multiplier_8bit

- Design Source VHDL Code of improved Multiplier_8bit

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity Multiplier_8bit is
    Port ( A : in STD_LOGIC_VECTOR (7 downto 0);
          B : in STD_LOGIC_VECTOR (7 downto 0);
          Ans : out STD_LOGIC_VECTOR (7 downto 0);
          Over_f : out STD_LOGIC;
          Zero : out STD_LOGIC);
end Multiplier_8bit;

architecture Behavioral of Multiplier_8bit is

    component Multiplier_4 is
        Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
              B : in STD_LOGIC_VECTOR (3 downto 0);
              Y : out STD_LOGIC_VECTOR (7 downto 0));
    end component;

    component RCA_4bit is
        Port (
            A : in STD_LOGIC_VECTOR (3 DOWNTO 0);
            B : in STD_LOGIC_VECTOR (3 DOWNTO 0);
            S : out STD_LOGIC_VECTOR (3 DOWNTO 0);
            C_in :in STD_LOGIC;
            C_out: out STD_LOGIC);
    end component;

    signal Mul_0_out,Mul_1_out,Mul_2_out,Mul_3_out : std_logic_vector(7 downto 0);
    signal add_1_0_out, add_1_1_out, add_2_0_out, add_2_1_out :std_logic_vector(3 downto 0);
    signal add_1_0_C, add_1_1_C, add_2_0_C, add_2_1_C : std_logic;
    signal Answer :std_logic_vector(7 downto 0);

begin

    Mul_4bit_0:Multiplier_4
    port map(
        A  => A(3 downto 0),
        B  => B(3 downto 0),
        Y  => Mul_0_out);    --- mul_0_out (3 downto zero is Ans( 3 downto 0)

    Mul_4bit_1:Multiplier_4
    port map(
        A  => A(7 downto 4),
        B  => B(3 downto 0),
        Y  => Mul_1_out);

    Mul_4bit_2:Multiplier_4
    port map(
        A  => A(3 downto 0),
        B  => B(7 downto 4),
        Y  => Mul_2_out);

    Mul_4bit_3:Multiplier_4
    port map(
        A  => A(7 downto 4),
        B  => B(7 downto 4),
        Y  => Mul_3_out);
```

```

--- Combining answers

ADDER_1_0:RCA_4bit
port map(
  A  => Mul_0_out(7 downto 4),
  B  => Mul_1_out(3 downto 0),
  S  => add_1_0_out,
  C_in => '0',
  C_out => add_1_0_C );

ADDER_1_1:RCA_4bit
port map(
  A  => add_1_0_out,
  B  => Mul_2_out(3 downto 0),
  S  => add_1_1_out,      --add_1_1_out is Ans( 7 downto 4)
  C_in => '0',
  C_out => add_1_1_C );

ADDER_2_0:RCA_4bit
port map(
  A  => Mul_1_out(7 downto 4),
  B  => Mul_2_out(7 downto 4),
  S  => add_2_0_out,
  C_in => add_1_0_C,
  C_out => add_2_0_C );

ADDER_2_1:RCA_4bit
port map(
  A  => add_2_0_out,
  B  => Mul_3_out(3 downto 0),
  S  => add_2_1_out,
  C_in => add_1_1_C,
  C_out => add_2_1_C );

Answer <= add_1_1_out & Mul_0_out (3 downto 0);

--outputs

Ans <= Answer;


Over_f <= add_2_1_C or add_2_0_C or add_2_1_out(0) or add_2_1_out(1) or add_2_1_out(2) or
add_2_1_out(3) or Mul_3_out(7) or Mul_3_out(6) or Mul_3_out(5) or Mul_3_out(4) or
add_1_1_out(3);

Zero <= not( Answer(0) or Answer(1) or Answer(2) or Answer(3) or Answer(4) or Answer(5) or
Answer(6) or Answer(7));

end Behavioral;

```

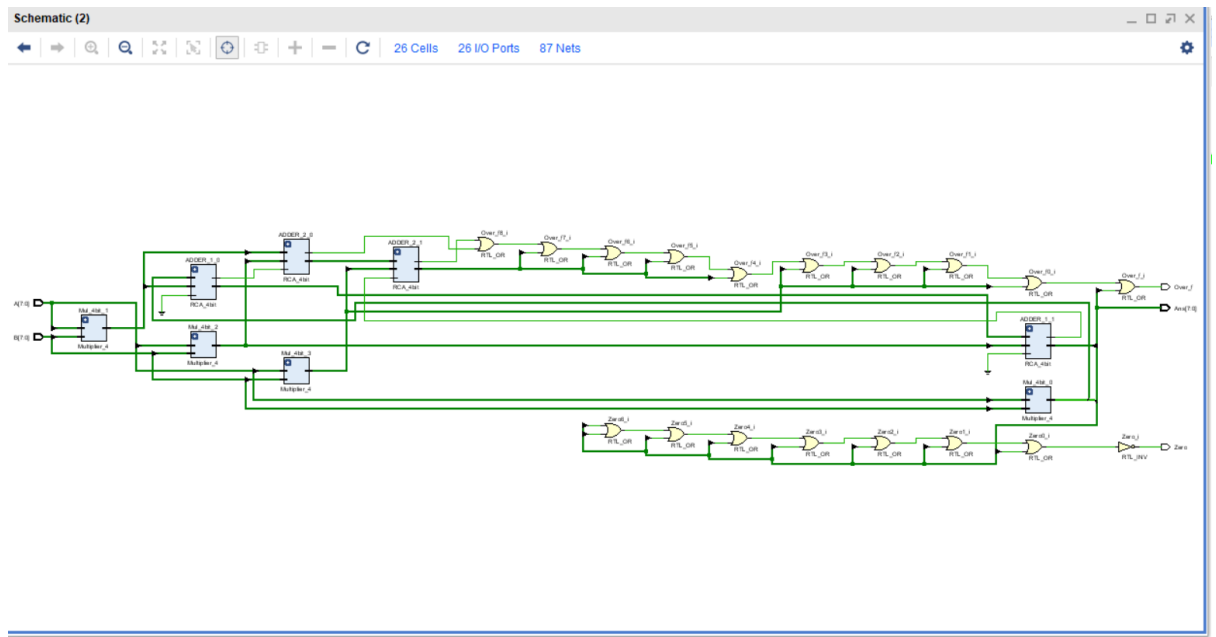- RTL Schematic Diagram of the improved Multiplier_8bit



- Behavioral Simulation Code for improved Multiplier_8bit

```
entity TB_Multiplier_8bit is
-- Port ( );
end TB_Multiplier_8bit;

architecture Behavioral of TB_Multiplier_8bit is

component Multiplier_8bit is
    Port ( A : in STD_LOGIC_VECTOR (7 downto 0);
          B : in STD_LOGIC_VECTOR (7 downto 0);
          Ans : out STD_LOGIC_VECTOR (7 downto 0);
          Over_f : out STD_LOGIC;
          Zero : out STD_LOGIC);
end component;

signal a, b, ans : STD_LOGIC_VECTOR (7 downto 0);
signal over_f ,zero : STD_LOGIC;

begin

    UUT :Multiplier_8bit
    port map(
        A  => a,
        B  => b,
        Ans => ans,
        Over_f => over_f,
        Zero  => zero);

    process
    begin

        a <= "00000000";
        b <= "00011101";
        wait for 100ns;

        a <= "00001000";
        b <= "00000101";
        wait for 100ns;

        a <= "00010000";
        b <= "00000011";
        wait for 100ns;

        a <= "11111000";
```

```

b <= "00011101";
wait for 100ns;

a <= "01010101";
b <= "00011101";
wait for 100ns;

a <= "11111100";
b <= "11111101";
wait for 100ns;

a <= "01000000";
b <= "00000001";
wait for 100ns;


a <= "00111100";
b <= "00000011";
wait;

end process;

```

end Behavioral;

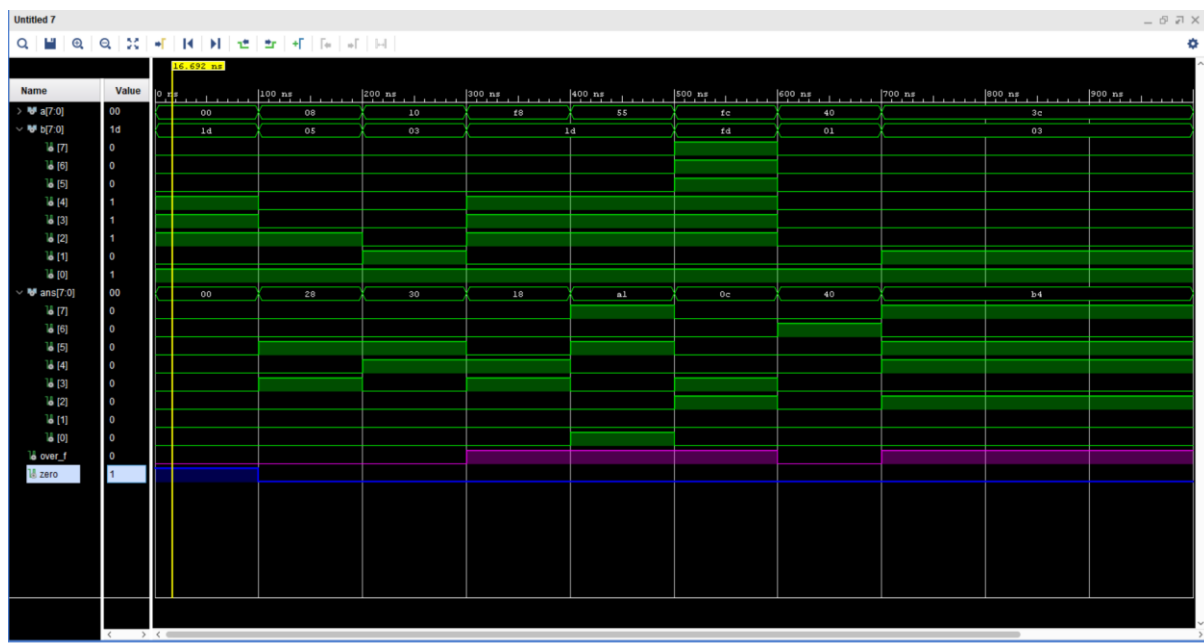- Timing Diagram for improved Multiplier_8bit



6. Program_ROM

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- arithmetic functions with Signed or Unsigned values
use IEEE.NUMERIC_STD.ALL;

entity Program_ROM is
    Port ( address : in STD_LOGIC_VECTOR (3 downto 0);
          data : out STD_LOGIC_VECTOR (16 downto 0));
end Program_ROM;

architecture Behavioral of Program_ROM is

    type rom_type is array (0 to 15) of std_logic_vector(16 downto 0);

    signal Program_ROM : rom_type := (
        "01011100000001010", -- MOVI R7,10
        "11101011100000000", -- COPY R2,R7
        "01000100000001100", -- MOVI R1,12
        "10011100100000000", -- MUL R7,R1
        "00111100000000000", -- NEG R7
        "00011101000000000", -- ADD R7,R2
        "01111100000001000", -- JZR R7,8
        "10100000000000101", -- JUMP 5
        "01001100000000001", -- MOVI R3,1
        "00101100000000000", -- NEG R3
        "01010000000001111", -- MOVI R4,15
        "00011101000000000", -- ADD R7,R2
        "00010001100000000", -- ADD R4,R3
        "11010000000001011", -- JNZ R4,11
        "01011100000100011", -- MOVI R7,35
        "01100000000001110" -- JZR R0,14
    );

begin
    data <= Program_ROM(to_integer(unsigned(address)));

end Behavioral;
```

7. LUT_16_7seg

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- arithmetic functions with Signed or Unsigned values
use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity LUT_16_7seg is
    Port ( value : in STD_LOGIC_VECTOR (7 downto 0);
          data_dis_0 : out STD_LOGIC_VECTOR (6 downto 0);
```

```

        data_dis_1 : out STD_LOGIC_VECTOR (6 downto 0);
        data_dis_2 : out STD_LOGIC_VECTOR (6 downto 0));
end LUT_16_7seg;

architecture Behavioral of LUT_16_7seg is

type rom_type is array (0 to 15) of std_logic_vector(6 downto 0);

    signal sevenSegment_ROM : rom_type := (
        "1000000", -- 0
        "1111001", --1
        "0100100",
        "0110000",
        "0011001", --4
        "0010010",
        "0000010", --6
        "1111000",
        "0000000",
        "0010000", --9
        "0001000", -- a
        "0000011",
        "1000110",
        "0100001",
        "0000110",
        "0001110" -- f
    );

signal abs_value : unsigned(7 downto 0);

begin

    process (value)
    begin
        abs_value <= unsigned(abs(signed(value)));

        data_dis_0 <= sevenSegment_ROM(to_integer(abs_value(3 downto 0)));
        data_dis_1 <= sevenSegment_ROM(to_integer(abs_value(7 downto 4)));

        if value(7)='0' then
            data_dis_2 <= "1111111";
        else
            data_dis_2 <= "0111111";
        end if;
    end process;

end Behavioral;

```

8. Constrain File

```
set_property PACKAGE_PIN W5 [get_ports {Clock}]
    set_property IOSTANDARD LVCMOS33 [get_ports {Clock}]
    create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports {Clock}]

## LEDs
set_property PACKAGE_PIN U16 [get_ports {R7_LED[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {R7_LED[0]}]
set_property PACKAGE_PIN E19 [get_ports {R7_LED[1]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {R7_LED[1]}]
set_property PACKAGE_PIN U19 [get_ports {R7_LED[2]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {R7_LED[2]}]
set_property PACKAGE_PIN V19 [get_ports {R7_LED[3]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {R7_LED[3]}]
set_property PACKAGE_PIN W18 [get_ports {R7_LED[4]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {R7_LED[4]}]
set_property PACKAGE_PIN U15 [get_ports {R7_LED[5]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {R7_LED[5]}]
set_property PACKAGE_PIN U14 [get_ports {R7_LED[6]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {R7_LED[6]}]
set_property PACKAGE_PIN V14 [get_ports {R7_LED[7]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {R7_LED[7]}]
set_property PACKAGE_PIN P1 [get_ports {Zero_LED}]
    set_property IOSTANDARD LVCMOS33 [get_ports {Zero_LED}]
set_property PACKAGE_PIN L1 [get_ports {Over_F_LED}]
    set_property IOSTANDARD LVCMOS33 [get_ports {Over_F_LED}]

##7 segment display
set_property PACKAGE_PIN W7 [get_ports {R7_7seg[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {R7_7seg[0]}]
set_property PACKAGE_PIN W6 [get_ports {R7_7seg[1]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {R7_7seg[1]}]
set_property PACKAGE_PIN U8 [get_ports {R7_7seg[2]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {R7_7seg[2]}]
set_property PACKAGE_PIN V8 [get_ports {R7_7seg[3]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {R7_7seg[3]}]
set_property PACKAGE_PIN U5 [get_ports {R7_7seg[4]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {R7_7seg[4]}]
set_property PACKAGE_PIN V5 [get_ports {R7_7seg[5]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {R7_7seg[5]}]
set_property PACKAGE_PIN U7 [get_ports {R7_7seg[6]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {R7_7seg[6]}]

set_property PACKAGE_PIN U2 [get_ports {Anode[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {Anode[0]}]
set_property PACKAGE_PIN U4 [get_ports {Anode[1]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {Anode[1]}]
set_property PACKAGE_PIN V4 [get_ports {Anode[2]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {Anode[2]}]
set_property PACKAGE_PIN W4 [get_ports {Anode[3]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {Anode[3]}]

##Buttons
set_property PACKAGE_PIN U18 [get_ports {Reset}]
    set_property IOSTANDARD LVCMOS33 [get_ports {Reset}]
```


◆ Contributions

Member	Individual Contribution	Worked Time
Jayasinghe J.D.D.S	<ul style="list-style-type: none"> • Instruction Decoder • Final Assembly Nano Processor & Simulation • Multiplier & Simulation, Instruction Decoder & Simulation, Final assembly & simulation, 7 segment Display in Improved version. 	4 hours 4 hours 5 hours
Rafi M.A.A	<ul style="list-style-type: none"> • ADD SUB Unit & Program ROM in basic version • Improved ADD SUB Unit • Improved Register Bank • 3 bit Adder 	3 hours 4 hour 2 hours
Kirindage S.S	<ul style="list-style-type: none"> • MUX 2 Way 4 bit • MUX 2 Way 3 bit • MUX 8 Way 4 bit • Simulation for Instruction Decoder in Basic Version • Finalizing Lab Report 	1 hour 1 hour 2 hours 2 hours 2 hours
Kariyapperuma K.M.N.S	<ul style="list-style-type: none"> • Simulation for Program Counter in Basic Version • Simulation Register Bank • Constraint files Basys3.xdc • Finalizing Lab Report • Simulation for Instruction Decoder in improved Version 	2 hours 2 hours 1 hour 1 hour 2 hours

◆ Conclusion

The nano processor design project was a culmination of everything we learned through our module and lab sessions. It taught us how to design individual components for specific functions and integrate them into a complete system to achieve a common goal. As a group project, it was a valuable experience in collaboration—sharing responsibilities, working together in harmony, and tackling challenges as a team.

We faced many obstacles, especially when combining components developed by different team members. Integrating these parts into a unified design required careful coordination and problem-solving. Throughout the journey, we embraced diverse ideas and made thoughtful decisions to refine our approach. Ultimately, we embedded our machine code into ROM, bringing our nano processor to life—a meaningful outcome shaped by teamwork, creativity, and perseverance.